


CMOS INVERTER

The CMOS Inverter – Static Model



Outline

- **First Glance**
- **Digital Gate Characterization**
- **Static Behavior (Robustness)**
 - **VTC**
 - **Switching Threshold**
 - **Noise Margins**


The CMOS Inverter: A First Glance

 

CMOS Inverters (1)

  

CMOS Inverter Operation Principle

 


$$V_{OH} = V_{DD} \quad V_{OL} = 0$$




Digital Gate Fundamental Parameters

- **Functionality**
- **Reliability, Robustness**
- **Area**
- **Performance**
 - **Speed (delay)**
 - **Power Consumption**
 - **Energy**

The Ideal Inverter

 


Static CMOS Properties

 

Basic inverter belongs to class of **static circuits**: output always connected to either V_{DD} or V_{SS} . **Not ideal but:**

 - Rail to rail voltage swing
- Ratio less design
- Low output impedance
- Extremely high input impedance
- No static power dissipation
- Good noise properties/margins




{TPS}: prioritize the list above

Voltage Transfer Characteristic (VTC)



Load Line (Ckt Theory)

 

Exercise:

The **blue** load line A corresponds to $R =$

The **orange** load line B corresponds to $R =$

With load line A and $V_{GS} = 1V$, $V_{out} =$

Draw a graph $V_{out}(V_{in})$ for load line A and B



PMOS Load Lines



Goal: Combine I_{Dn} and I_{Dp} in one graph

Kirchoff:

$$V_{in} = V_{DD} + V_{GSp}$$

$$I_{Dn} = -I_{Dp}$$

$$V_{out} = V_{DD} + V_{DSp}$$

  


Example: $V_{DD} = 5V$

$$V_{in} = V_{DD} + V_{GSp}$$



$$I_{Dn} = -I_{Dp}$$

$$V_{out} = V_{DD} + V_{DSp}$$

CMOS Inverter Load Characteristics

 


CMOS Inverter VTC

  

Operating Conditions

 Need to know for proper dimensioning, analysis of noise margin, etc.



Exercise: check results for PMOS


NMOS

- 1 $V_{in} = V_{GS} < V_{Tn} \Rightarrow$ **off**
- 2 $V_{out} > V_{in} - V_{Tn}$
 $V_{DS} > V_{GS} - V_{Tn}$
 $V_{GD} < V_{Tn} \Rightarrow$ **saturation**
- 3 $V_{out} < V_{in} - V_{Tn} \Rightarrow$ **resistive**


PMOS

- 4 $V_{in} > V_{DD} + V_{Tp} \Rightarrow$ **off**
- 5 $V_{out} < V_{in} - V_{Tp} \Rightarrow$ **saturation**
- 6 $V_{out} > V_{in} - V_{Tp} \Rightarrow$ **resistive**

Operating Conditions

 

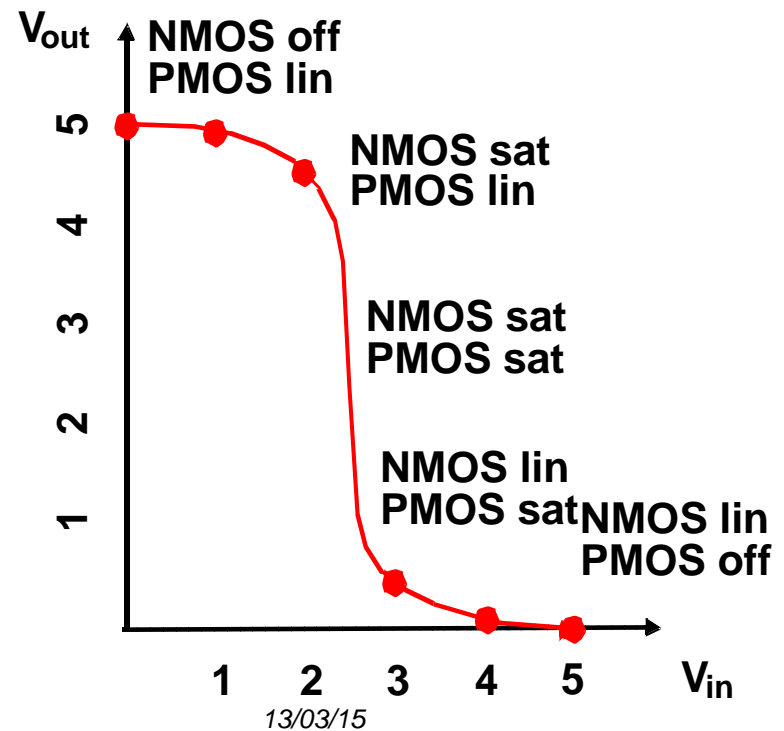NMOS 1 off 2 saturation 3 resistive
PMOS 4 off 5 saturation 6 resistive





Inverter Static Behavior


- Regeneration
- Noise margins
- Delay metrics




The Realistic Inverter

 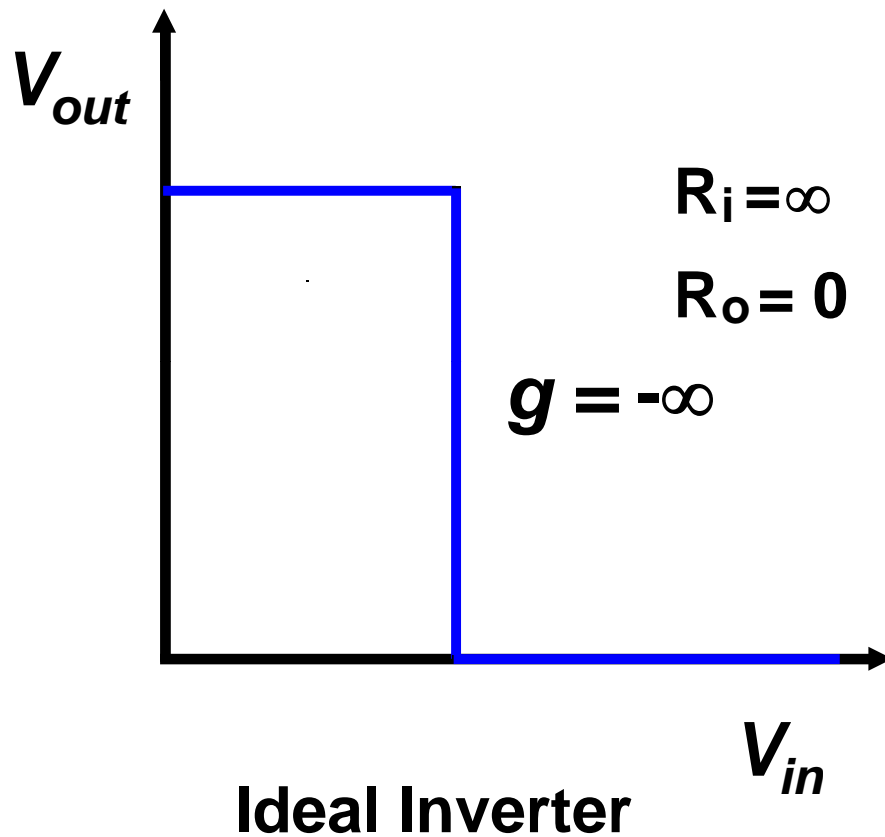

The Regenerative Property

 


A chain of inverters

 


■ **Regenerative Property:** ability to regenerate (repair) a weak signal in a chain of gates


The regenerative property

 


The Regenerative Property (2)

 

(a) A chain of inverters.

 


(b) Regenerative gate

 

(c) Non-regenerative gate

The regenerative Property (3)

 


Exercise: what is the output voltage of a chain of 4 inverters with a piece-wise linear VTC passing through (0, 10), (3,7), (7,1) and (10,0) [Volt], as the result of an input voltage of 6 [Volt].

 Exercise: discuss the behavior for an input of 5 [Volt]


Inverter Switching Threshold

- Not the device threshold $V_m = f(R_{onn}, R_{onp})$
- Point of $V_{in} = V_{out}$




- Try to set W_n, L_n, W_p, L_p so that VTC is symmetric as this will improve noise margins

optimize NMOS-PMOS ratio

 

Simulated Gate Switching Threshold

 

Electrical Design Rule

$$W_p \approx 2.5 W_n$$

- Assumes $L_p = L_n$
- Should be applied consistently

■ Symmetrical VTC $\Rightarrow V_m \approx \frac{1}{2} V_{DD} \Rightarrow W_p/W_n \approx$



■ In practice: somewhat smaller

■ Why?

Inverter Switching Threshold

Analytical Derivation

  - V_M is V_{in} such that $V_{in} = V_{out}$
- $V_{DS} = V_{GS} \Leftrightarrow V_{GD} = 0 \Rightarrow$ saturation
 - Assume $V_{DSAT} < V_M - V_T$
 - (velocity saturation)
 - Ignore channel length modulation
- V_M follows from
 - $I_{DSATn}(V_M) = -I_{DSATp}(V_M)$



Inverter Switching Threshold

Analytical Derivation (ctd)

$$I_{DSATn}(V_M) = -I_{DSATp}(V_M)$$

$$I_D = kV_{DSAT}(V_{GS} - V_T - V_{DSAT}/2)$$

$$\Leftrightarrow k_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2) = -k_p V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)$$

$$\Leftrightarrow \frac{k_p}{k_n} = \frac{-V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)} \quad k = \frac{W}{L} k'$$

$$\Rightarrow \frac{(W/L)_p}{(W/L)_n} = \left| \frac{k'_n V_{DSATn} (V_M - V_{Tn} - V_{DSATn}/2)}{k'_p V_{DSATp} (V_M - V_{DD} - V_{Tp} - V_{DSATp}/2)} \right|$$


■ See Example 5.1:

■ $(W/L)_p = 3.5 (W/L)_n$ for typical conditions and $V_M = \frac{1}{2} V_{DD}$

■ Usually: $L_n = L_p$

Gate Switching Threshold w/o Velocity Saturation

 
- Long channel approximation
- Also applicable with low V_{DD}



Exercise (Problem 5.1):
derive V_M for long-
channel approximation
as shown below

$$V_M = \frac{r(V_{DD} - V_{Tp} + V_{Tn})}{1+r} \text{ with } r = \sqrt{\frac{-k_p}{k_n}}$$



Noise in Digital Integrated Circuits

 


(a) Inductive coupling (b) Capacitive coupling (c) Power and ground noise

- Study behavior of static CMOS Gates with **noisy signals**

Noise in Digital Circuits

  


Noise Margins

 



- V_{OL} = Output Low Voltage
- V_{IL} = Input Low Voltage
- $V_{OH}, V_{IH} = \dots$

Noise Margins

 

- V_{OL} = Output Low Voltage
- V_{IL} = Input Low Voltage
- $V_{OH}, V_{IH} = \dots$


Noise Margins

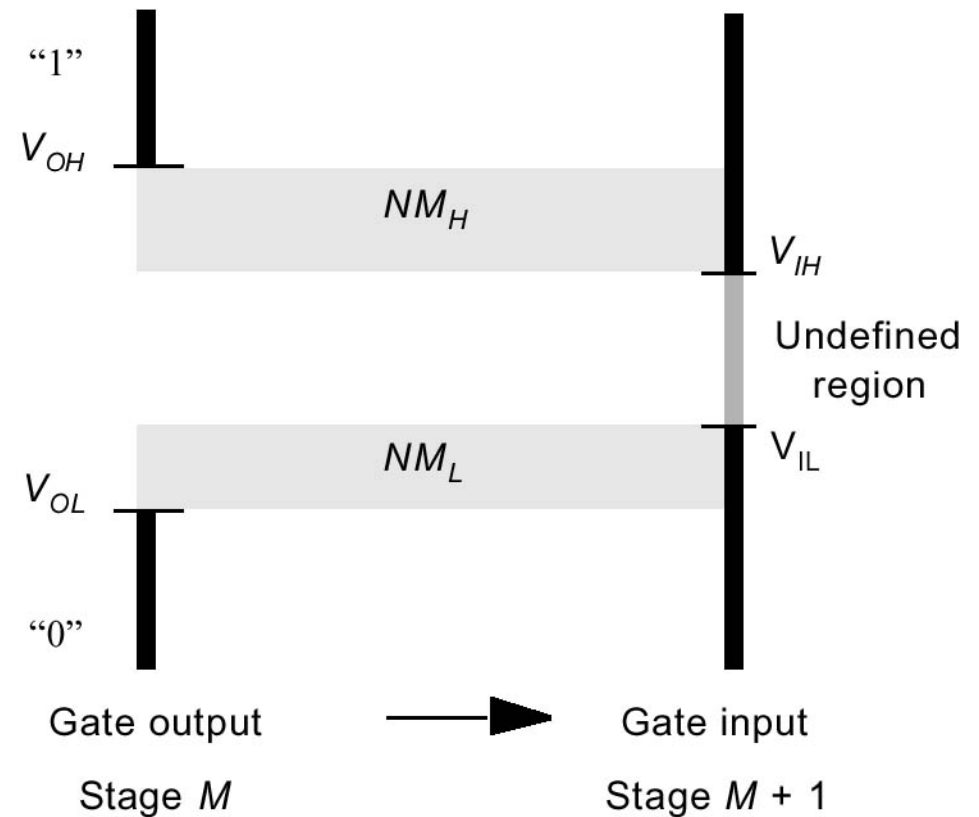 

■ $NM_H = V_{OH} - V_{IH} = \text{High Noise Margin}$

■ $NM_L = V_{IL} - V_{OL} = \text{Low Noise Margin}$


Noise Margin for Realistic Gates

 

- V_{OL} not well defined
- Conveniently relate to slope $s = -1$

{TPS}: explain significance of slope = -1 for noise margin

Noise Margin Calculation

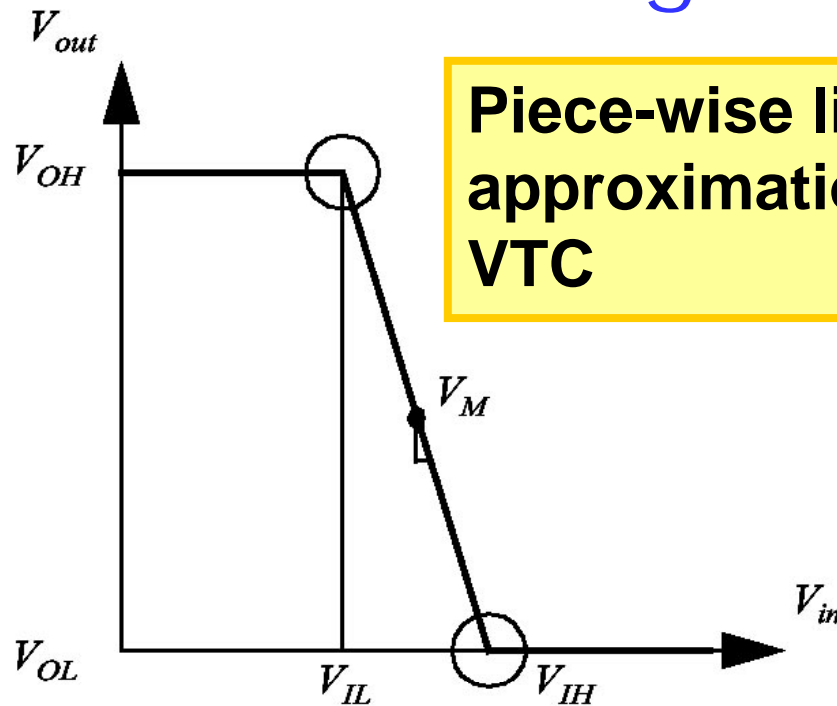

Piece-wise linear approximation of VTC

g = gain factor (slope of VTC)

We know how to compute V_M
Next: how to compute g

$$V_{IH} - V_{IL} = -\frac{(V_{OH} - V_{OL})}{g} = \frac{-V_{DD}}{g}$$

$$V_{IH} = V_M - \frac{V_M}{g} \qquad V_{IL} = V_M + \frac{V_{DD} - V_M}{g}$$

$$NM_H = V_{DD} - V_{IH} \qquad NM_L = V_{IL}$$

Noise Margin Calculation (2)

- Approximate g as the slope in V_{out} vs. V_{in} at $V_{in} = V_M$

$$k_n V_{DSATn} (V_{in} - V_{Tn} - V_{DSATn} / 2)(1 + \lambda_n V_{out}) +$$

$$k_p V_{DSATp} (V_{in} - V_{DD} - V_{Tp} - V_{DSATp} / 2)(1 + \lambda_p V_{out} - \lambda_p V_{DD}) = 0$$



$$g = \left. \frac{dV_{out}}{dV_{in}} \right|_{V_{in}=V_M} \approx \frac{1+r}{(V_M - V_T - V_{DSATp} / 2)(\lambda_n - \lambda_p)} \quad r = \frac{k_p V_{DSATp}}{k_n V_{DSATn}}$$

- Mostly determined by technology
- See example 5.2

- **Exercise:** verify calculation
- **Exercise:** explain why we add channel length modulation to the I_D expressions (we did not do this to determine V_M)

Gain as a function of VDD


consider $g = \left. \frac{dV_{out}}{dV_{in}} \right|_{V_{in}=V_M} \approx \frac{1+r}{(V_M - V_T - V_{DSATp}/2)(\lambda_n - \lambda_p)}$

  

Subthreshold!

Dynamic Noise Margin

 - Previous definition was **Static Noise Margin**
- **Dynamic Noise Margin**: how does noise energy determine behavior
- A short pulse may have higher amplitude than a long pulse before problems occur.
- Short spikes may safely exceed **Static Noise Margin**



CMOS INVERTER

dynamic behavior (performance)


- **Capacitances**
- **(Dis)charge times**
- **Delay**



■ Before: propagation delay analysis

$$t_p \approx 0.69 \times \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right) C_L$$

 ■ Next: propagation delay from a design perspective inverter sizing



The Transistor as a Switch

$V_{GS} \geq V_T$

Ex. 3.8


$$R_{eq} = \frac{1}{2} \left(\frac{V_{DD}}{I_{DSAT}(1 + \lambda V_{DD})} + \frac{V_{DD}/2}{I_{DSAT}(1 + \lambda V_{DD}/2)} \right) \approx \frac{3}{4} \frac{V_{DD}}{I_{DSAT}} \left(1 - \frac{5}{6} \lambda V_{DD} \right)$$

TUD/EE ET4293 - Dig. IC - 1112 - © NvdM - 01 Devices
12/03/05
39

Reducing t_p

$$t_{pHL} \approx 0.69 \times \frac{3}{4} \frac{V_{DD}}{I_{DSATn}} \left(1 - \frac{5}{6} \lambda V_{DD} \right) C_L$$

$$I_{DSAT} = k' \frac{W}{L} \left[(V_{GS} - V_T) V_{DSAT} - \frac{1}{2} V_{DSAT}^2 \right]$$

$\lambda=0$


$$t_{pHL} \approx 0.52 \frac{C_L V_{DD}}{(W/L)_n k'_n V_{DSATn} (V_{DD} - V_{Tn} - V_{DSATn}/2)}$$

{TPS}: How can you reduce propagation delay?

Propagation Delay t_p can be reduced by

- Increasing V_{DD} (until $V_{DD} \gg V_T + V_{DSAT}/2$)
- Increasing W
- Reducing C_L

Delay as a function of V_{DD}

 


Fig.5.17

Sizing


Propagation Delay t_p can be reduced by

- Increasing V_{DD} (until $V_{DD} \gg V_T + V_{DSAT}/2$)
- Increasing W
- Reducing C_L

$$t_{pHL} = 0.52 \frac{C_L V_{DD}}{(W/L)_n k_n' V_{DSATn} (V_{DD} - V_{Tn} - V_{DSATn}/2)} \propto \frac{C_L}{W}$$

- C_L can be reduced by good layout design
- But part of C_L depends on W !



t_p as a function of W_p/W_n

 


$W_n \uparrow$ {
 $\Rightarrow I_{pd} \uparrow \Rightarrow t_{pHL} \downarrow$
 $\Rightarrow C_D \uparrow \Rightarrow t_{pLH} \uparrow$

$W_p \uparrow$ {
 \dots
 \dots

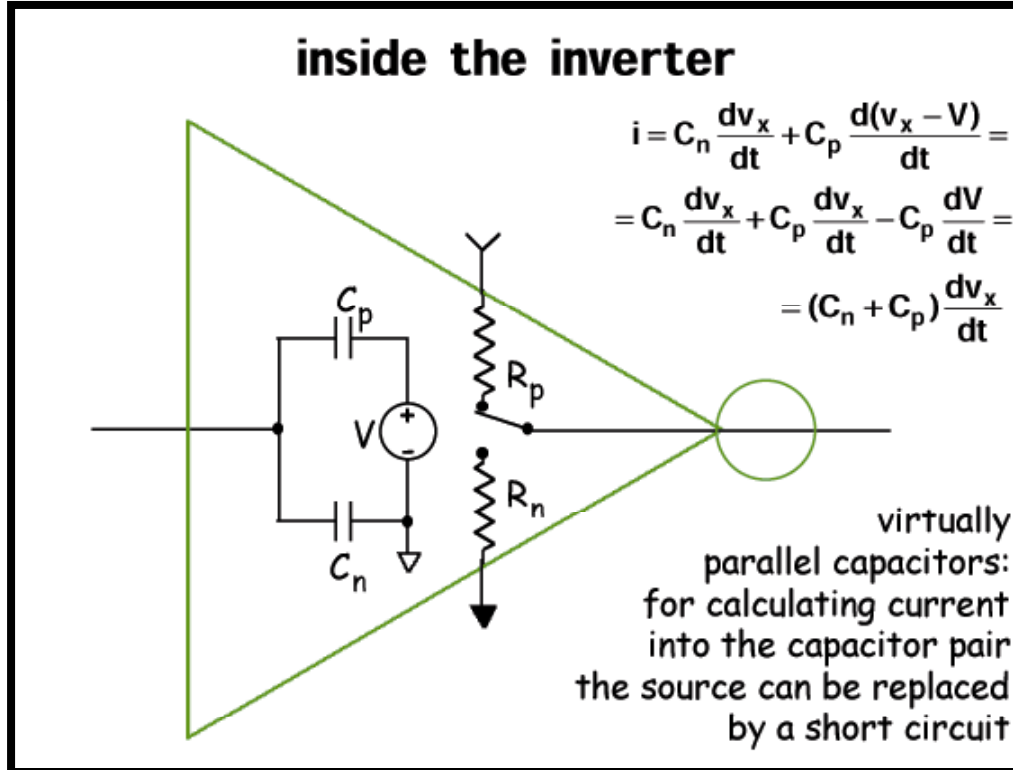 Min t_p in general not when $t_{pLH} = t_{pHL}$
Save area, time at expense of robustness



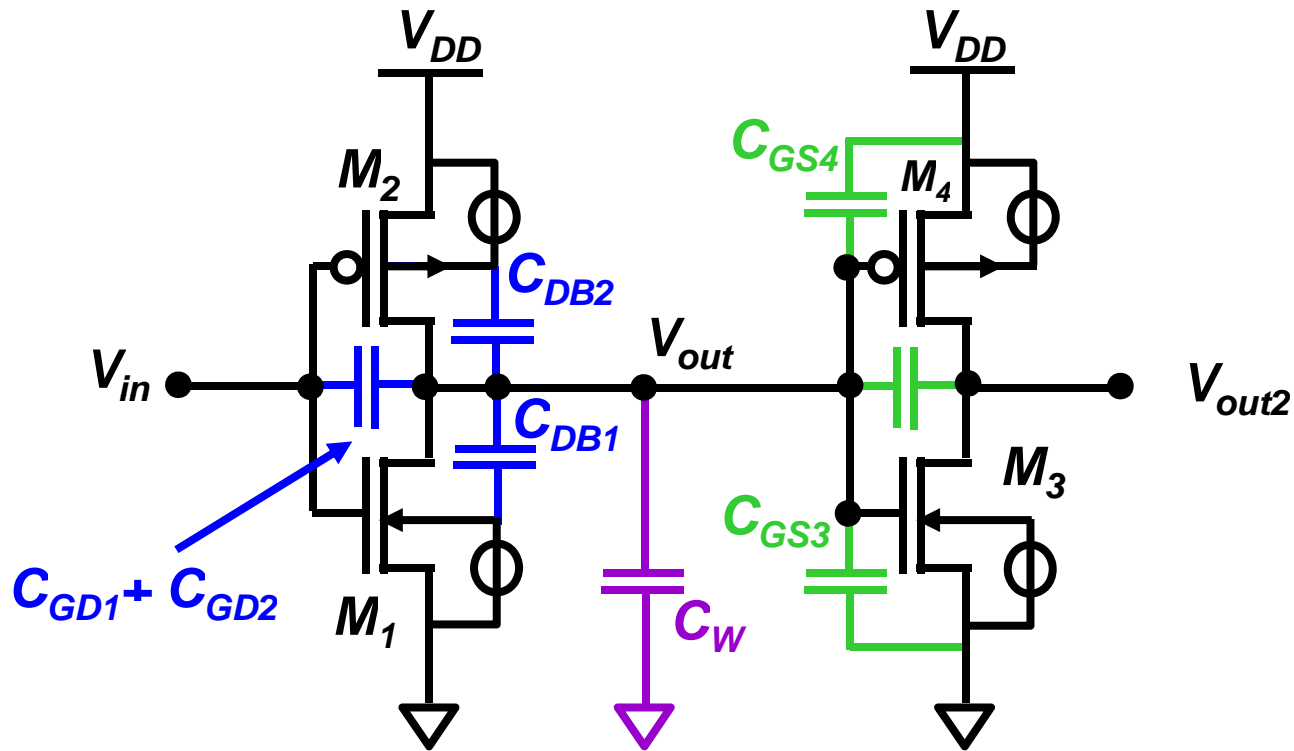Intrinsic vs Extrinsic vs Parasitic Load Cap



- $C_{int} = C_{DB1} + C_{DB2} + 2(C_{GD1} + C_{GD2})$

- $C_{ext} = C_{GS3} + C_{GS4} + C_{GD3} + C_{GD4}$

- $C_{par} = C_w$

Intrinsic load

Extrinsic / fan-out load

Parasitic load

Isolated Inverter Sizing

$$t_p = 0.69 R_{eq} (C_{int} + C_{ext}) = 0.69 R_{eq} C_{int} \left(1 + \frac{C_{ext}}{C_{int}} \right)$$

Assume C_{par} can be ignored or its effect can be absorbed in other C

R_0 : resistance of minimum size inverter
(assume proper $\beta = W_p / W_n$ ratio)

C_0 : intrinsic load (output, drain) cap of min. size inverter

$$t_{p0} = 0.69 R_0 C_0$$

intrinsic or unloaded delay

basic time constant for technology

minimum delay possible in technology given V_{DD}

S : sizing factor for W_n , W_p of driving inverter

$$W_n = S W_{min}, W_p = S \beta W_{min}$$

$$\rightarrow R_{eq} = R_0 / S$$


$$C_{int} = S C_0$$

$$\Rightarrow t_p = t_{p0} \left(1 + \frac{C_{ext}}{S C_0} \right)$$

Isolated Inverter Sizing

$$t_p = t_{p0} \left(1 + \frac{C_{ext}}{SC_0} \right)$$

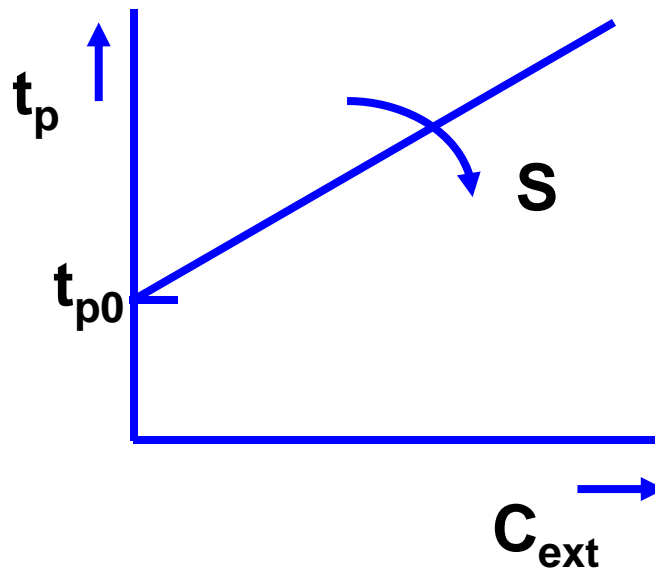
Increasing S reduces delay until $SC_0 \gg C_{ext}$



Inverter Chain

Assume size of inverter 1 is fixed.

 - ☺ Increasing S of inverter 2 reduces t_p of inverter 2
- ☹ But it increases t_p of inverter 1 (higher load cap)
- ☺ Expect an optimum!



{TPS} If C_L is given and knowing properties of input source:
- How many stages are needed to minimize the delay?
- How to size the inverters?

Delay Formula

$$t_p = t_{p0} \left(1 + \frac{C_{ext}}{SC_0} \right) = t_{p0} \left(1 + \frac{f}{\gamma} \right)$$

C_{gin} input gate capacitance

$$\gamma = C_{int}/C_{gin} = SC_0/C_{gin}$$


self loading coefficient

property of technology, typically $\gamma \approx 1$

$f = C_{ext}/C_{gin}$ effective fanout

$$\frac{f}{\gamma} = \frac{C_{ext}}{C_{gin}} \times \frac{C_{gin}}{SC_0}$$

Apply to Inverter Chain

 

$$t_p = t_{p,1} + t_{p,2} + \dots + t_{p,N}$$

$$t_{p,j} = t_{p0} \left(1 + \frac{f_j}{\gamma} \right) = t_{p0} \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right)$$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{j=1}^N \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right), \quad C_{gin,N+1} = C_L$$

$$[t_p = t_{p0}(1+f/\gamma)]$$

$$[f = C_{ext}/C_{gin} \text{ effective fanout}]$$

Apply to Inverter Chain

Delay equation has $N-1$ unknowns, $C_{gin,2} \dots C_{gin,N}$

$$t_p = \sum_{j=1}^N t_{p,j} = t_{p0} \sum_{j=1}^N \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right), \quad C_{gin,N+1} = C_L$$

Make $N-1$ partial derivatives for $C_{gin,j}$ zero for minimization:

$$\frac{\partial t_p}{\partial C_{gin,j}} = t_{p0} \left(\frac{1}{\gamma C_{gin,j-1}} - \frac{C_{gin,j+1}}{\gamma (C_{gin,j})^2} \right) = 0, \quad j = 2 \dots N-1$$

$$\frac{1}{a} = \frac{b}{c^2} \Leftrightarrow c = \sqrt{ab}$$

Optimal size of each stage is geometric mean of 2 neighbors:

$$C_{gin,j} = \sqrt{C_{gin,j-1} \times C_{gin,j+1}}, \quad j = 2 \dots N-1$$

Optimal Tapering for Given N

Optimal size of each stage is geometric mean of 2 neighbors:

$$C_{gin,j} = \sqrt{C_{gin,j-1} \times C_{gin,j+1}}, \quad j = 2 \dots N-1$$

⇒ $C_{gin,j}^2 = C_{gin,j-1} \times C_{gin,j+1}$

⇒ $\frac{C_{gin,j}}{C_{gin,j-1}} = \frac{C_{gin,j+1}}{C_{gin,j}}$


Load cap / input cap ratio
same for each stage

⇒ $f_j = \frac{C_{gin,j+1}}{C_{gin,j}} = N \sqrt{\frac{C_L}{C_{gin,1}}} = N \sqrt{F}$

$F = C_L / C_{gin,1}$: path fan-out.
Same fan-out, same delay for
each stage.

⇒ $t_{p,j} = t_{p0} \left(1 + \frac{f_j}{\gamma} \right) = t_{p0} \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right) = t_{p0} \left(1 + \frac{N \sqrt{F}}{\gamma} \right)$

Optimal Tapering for Fixed-N Summary

 

Delay per stage and total Path Delay

$$t_{p,j} = t_{p0} \left(1 + \frac{f_j}{\gamma} \right) = t_{p0} \left(1 + \frac{C_{gin,j+1}}{\gamma C_{gin,j}} \right) = t_{p0} \left(1 + \frac{N\sqrt{F}}{\gamma} \right)$$


$$t_p = N t_{p0} \left(1 + \frac{f_j}{\gamma} \right)$$

$$f_1 = f_2 = f_3 = \dots = F^{1/N}$$

$$f_1 \times f_2 \times f_3 \times \dots = F$$

$$F = C_L / C_{gin,1}$$

Example

 

C_L/C_1 has to be evenly distributed across $N = 3$ stages:

$$f = \sqrt[3]{8} = 2 \qquad t_p = 3t_{p0} \left(1 + \frac{\sqrt[3]{8}}{\gamma} \right) = 9t_{p0} \quad \text{for } \gamma = 1$$

Optimum Number of Stages

For a given load, C_L and given input capacitance C_{in}

find optimal f if N is free (and possibly non-integer)

$$C_L = F \cdot C_{in} = f^N C_{in} \quad \text{with} \quad N = \frac{\ln F}{\ln f}$$

$$t_p = N t_{p0} \left(1 + \frac{f}{\gamma} \right) = \frac{t_{p0} \ln F}{\gamma} \left(\frac{\gamma}{\ln f} + \frac{f}{\ln f} \right)$$

$$\frac{\partial t_p}{\partial f} = \frac{t_{p0} \ln F}{\gamma} \cdot \frac{-\gamma/f + \ln f - 1}{\ln^2 f} = 0$$

$$\ln f = 1 + \frac{\gamma}{f}$$

$$f = \exp\left(1 + \frac{\gamma}{f}\right)$$

**Closed-form solution
only for $\gamma = 0$**


Optimum Effective Fanout f

Optimum f for given process defined by γ


$$f = \exp\left(1 + \frac{\gamma}{f}\right) \quad N = \frac{\ln F}{\ln f}$$

(In practice, N must be rounded up or down to integer value)

	$\gamma=0$	$\gamma=1$
f_{opt}	$e=2.72$	3.6
N_{opt}	$\ln F$	$0.78 \ln F$

 

Normalized t_p vs. f

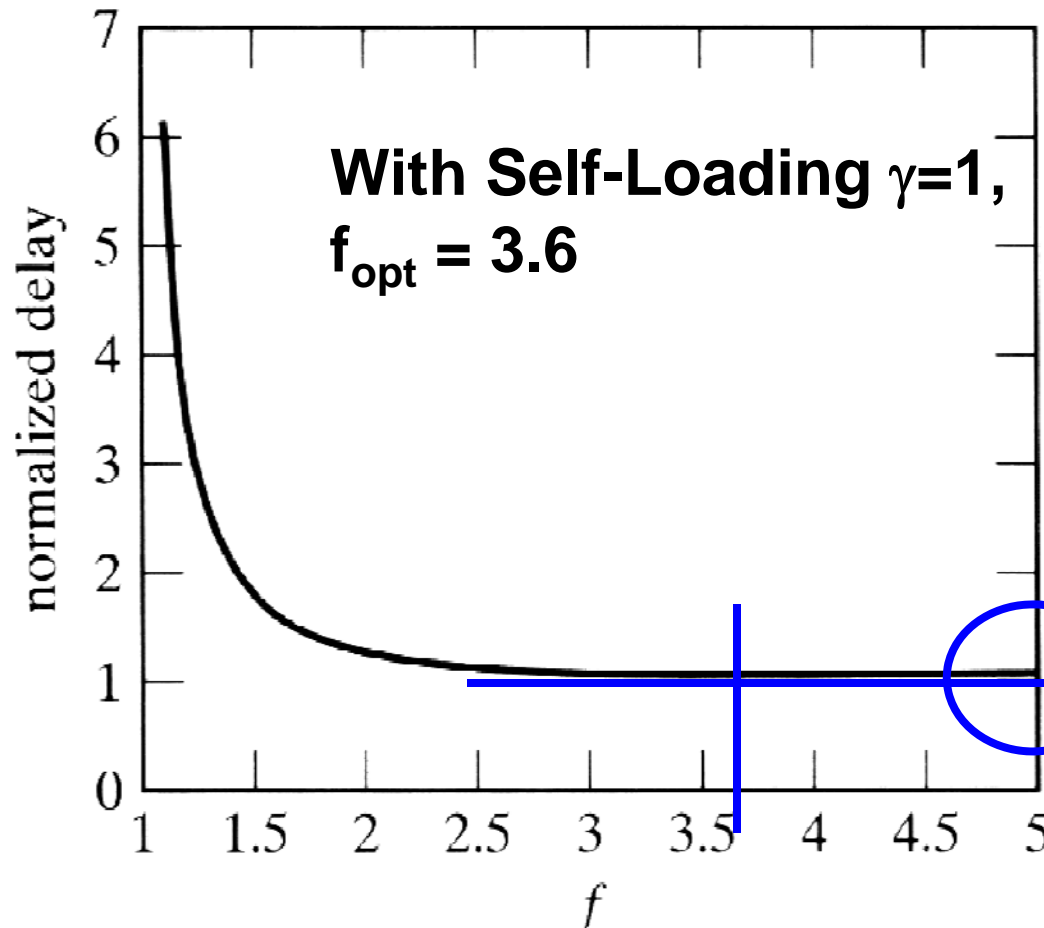

- Slight increase of t_p for $f > f_{opt}$
- Choosing too few stages ($f > f_{opt}$) is relatively harmless for delay and saves area
- Too many stages is expensive in terms of delay

Fan-out of 4 (FO4) is safe common practice


<http://en.wikipedia.org/wiki/FO4>

Normalized delay function of F

$$t_p = Nt_{p0} \left(1 + \frac{\sqrt[N]{F}}{\gamma} \right) \quad (\gamma = 1)$$

F	Unbuffered	Two Stage	Inverter Chain
10	11	8.3	8.3
100	101	22	16.5
1000	1001	65	24.8
10,000	10,001	202	33.1

Buffer Design

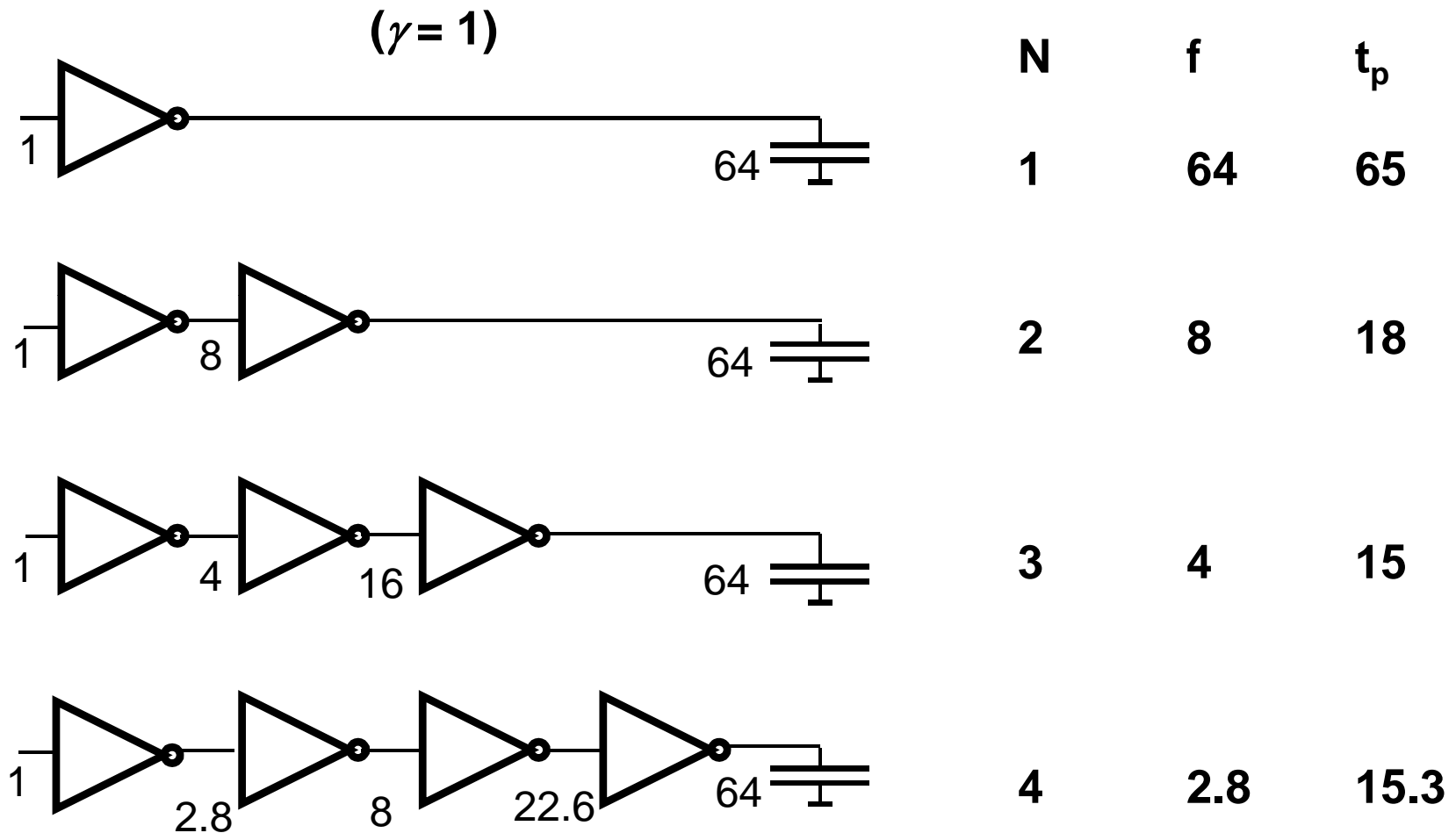

Power

- Dynamic Power
- Static Power
- Metrics



www.quietpc.com



**24 hours audio
playback time**

CMOS Power Dissipation

- Power dissipation is a **very important** circuit characteristic
- CMOS has relatively low static dissipation
- Power dissipation was the reason that CMOS technology won over bipolar and NMOS technology for digital IC's
- (Extremely) high clock frequencies increase dynamic dissipation
- Low V_T increases leakage
- Advanced IC design is a continuous struggle to contain the power requirements!



Power Density




Estimate

- Furnace: 2000 Watt, $r=10\text{cm}$ → $P \approx 6\text{Watt/cm}^2$
- Processor chip: 100 Watt, 3cm^2 → $P \approx 33\text{Watt/cm}^2$

Power-aware design, design for low power, is blossoming subfield of VLSI Design

- **{TPS}**: what is the difference in power between Bipolar and CMOS technologies?
- **A: 10 years**

 
Power Evolution over Technology Generations



Introduction of CMOS over bipolar bought industry 10 years
(example: IBM mainframe processors)

[From: Jan Rabaey, Low Power Design Essential, Ref: R. Chu, JEP'04]

Low Power Design Essentials

 

SpringerLink - Book - Mozilla Firefox
http://www.springerlink.com/content/116e9h2/

SpringerLink
Try the new SpringerLink Beta

TU Delft
Delft University of Technology

Institutional Login
Recognized as:
Technische Universiteit Delft (150-40-965)
UKB Netherlands OJA 2005-2009 (127-79-678)
1263 UKB Netherlands LNM (191-45-973)
1261 UKB Netherlands LNP (445-61-068)
1254 UKB Netherlands Landolt Börnstein (577-14-382)
1260 UKB Netherlands LNCS incl. archives (592-86-894)
1034 UKB (593-67-639)
UKB Netherlands LNES (617-63-136)
UKB Netherlands Brill (711-55-095)

Content Types Subject Collections
Book

Low Power Design Essentials

Book Series	Integrated Circuits and Systems
ISSN	1558-9412
Subject	Engineering, Electrical Engineering and Circuits a
Publisher	Springer US
DOI	10.1007/978-0-387-71713-5
Copyright	2009
ISBN	978-0-387-71712-8 (Print) 978-0-387-71713-5 (
Subject Collection	Engineering
Subject	Engineering, Electrical Engineering and Circuits a
SpringerLink Date	Tuesday, April 21, 2009

Editorial View Condensed List View Expanded List View

13 Chapters

- Front Matter
PDF (431.3 KB)
- Chapter
Introduction
Jan Rabaey
DOI: 10.1007/978-0-387-71713-5_1
PDF (2.4 MB) HTML
- Chapter
Nanometer Transistors and Their Models
Jan Rabaey
DOI: 10.1007/978-0-387-71713-5_2

- Recommended reading
(available online via University Library and [site \(?\)](#) of book)

Where Does Power Go in CMOS

- **Dynamic Power Consumption**
 - Charging and discharging capacitors**
- **Short Circuit Currents**
 - Short circuit path between supply rails during switching (NMOS and PMOS on together)**
- **Leakage**
 - Leaking diodes and transistors**
 - May be important for battery-operated equipment**

Dynamic Power

Dynamic Power


- E_i = energy of switching event i
 - independent of switching speed
 - depends on process, layout

- Power = Energy/Time

$$P = \frac{1}{T} \sum_i E_i$$

- E_i = Power-Delay-Product P-D
 - important quality measure
- Energy-Delay-Product E-D
 - combines power*speed performance

Low-to-High Transition Energy

 

Equivalent circuit for **low-to-high** transition


E_C - Energy stored on C

$$E_C = \int_0^{\infty} i v_0 dt \quad v_0 = v_0(t) \quad i = i(t) = C \frac{dv_0}{dt}$$

$$= \int_0^{\infty} C v_0 \frac{dv_0}{dt} dt$$

$$= \int_0^{V_{DD}} C v_0 dv_0 = \frac{1}{2} C v_0^2 \Big|_0^{V_{DD}} = \frac{1}{2} C V_{DD}^2$$

Low-to-High Transition Energy

 

$E_{V_{DD}}$ Energy delivered by supply


$$E_{V_{DD}} = \int_0^{\infty} i(t) V_{DD} dt = \int_0^{V_{DD}} C V_{DD} \frac{dv_0}{dt} dt = C V_{DD}^2$$

$$E_{V_{DD}} = C V_{DD}^2 \quad E_C = \frac{1}{2} C V_{DD}^2$$

Where is the rest?



Low-to-High Transition Energy

 


E_{diss} Energy dissipated in transistor

$$\begin{aligned} E_{diss} &= \int_0^{\infty} i(V_{DD} - v_0) dt \\ &= \int_0^{\infty} iV_{DD} dt - \int_0^{\infty} iv_0 dt \\ &= E_{V_{DD}} - E_C \end{aligned}$$



High-to-Low Transition Energy

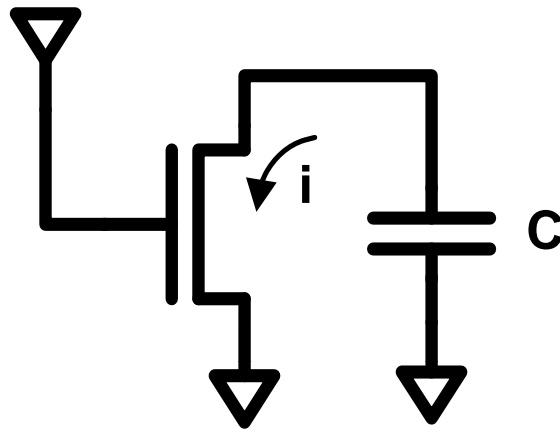


Equivalent circuit

Exercise: Show that the energy that is dissipated in the transistor upon discharging C from V_{DD} to 0 equals $E_{\text{diss}} = \frac{1}{2}CV_{DD}^2$

Compare Charging Strategies

Constant voltage

$$i = C \frac{dV_C}{dT}$$

 


$$E_R = \int_0^{\infty} V_R i dt = \int_0^{\infty} (V - V_C) C \frac{dV_C}{dt} dt$$

$$= \int_0^V (V - V_C) C dV_C = \frac{1}{2} CV^2$$

Constant current

$$I = \frac{CV}{T}$$

 

$$E_R = \int_0^{\infty} I(RI) dt = \int_0^T I(RI) dt = RI^2 T$$

$$= \frac{RC}{T} CV^2$$


- Reduced dissipation if $T > 2RC = t_{76\%}$
- Difficult to reap benefits in practice
- See 'Adiabatic Logic'

CMOS Dynamic Power Dissipation

$$\begin{aligned} \text{Power} &= \frac{\text{Energy}}{\text{Time}} = \frac{\text{Energy}}{\text{transition}} \times \frac{\#\text{transitions}}{\text{time}} \\ &= CV_{DD}^2 \times f \end{aligned}$$


- Independent of transistor on-resistances
- Can only reduce C , V_{DD} or f to reduce dynamic power

Short Circuit Current

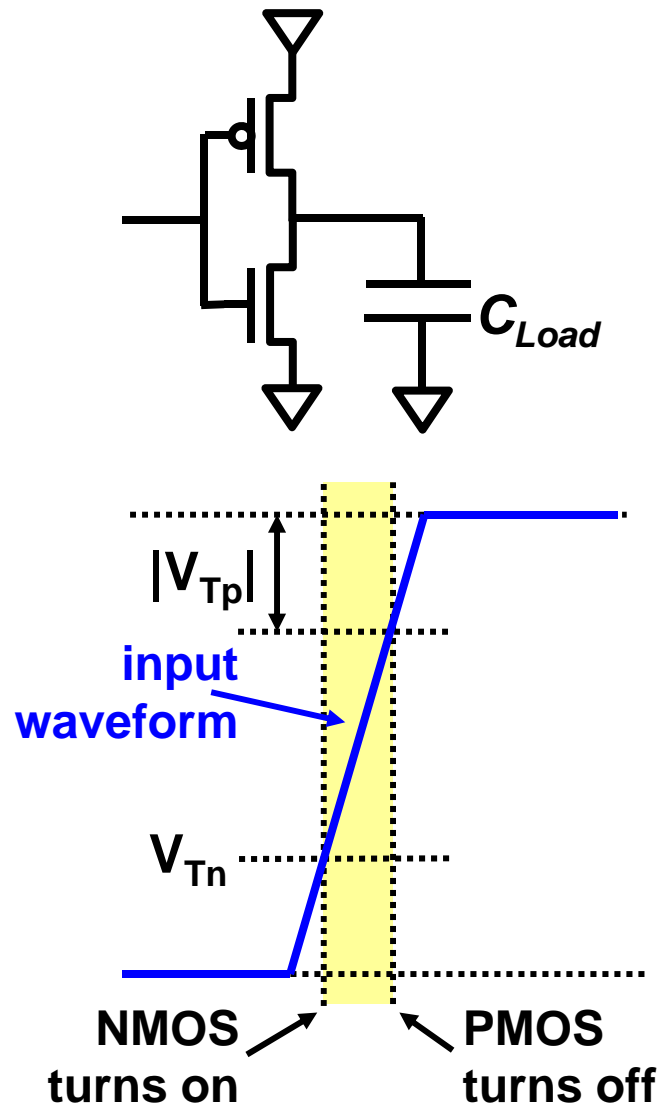


- Shaded area is where both pull-up and pull-down transistors are on (this is when short-circuit current can exist). This region is determined by crossings of input waveform with V_{Tn} and $V_{DD} - |V_{Tn}|$.
- Short circuit current for output going low is the current delivered by the PMOS
 - (NMOS current is used for discharging)
- {TPS} Discuss the influence of C_{Load} on the amount of short circuit dissipation
higher $C_{LOAD} \rightarrow$ higher dissipation?
or not?

Short Circuit Current

 


- **Input** and **output** waveforms of inverter loaded with a large capacitance (top) and with a small capacitance (bottom).
- Short-circuit current increases with $|V_{DSpl}|$. This is clearly much larger on average for small C_L compared to large C_L .
- Similarly, short-circuit current can exist for low-to-high transition at output.

Short Circuit Current

 


Large load

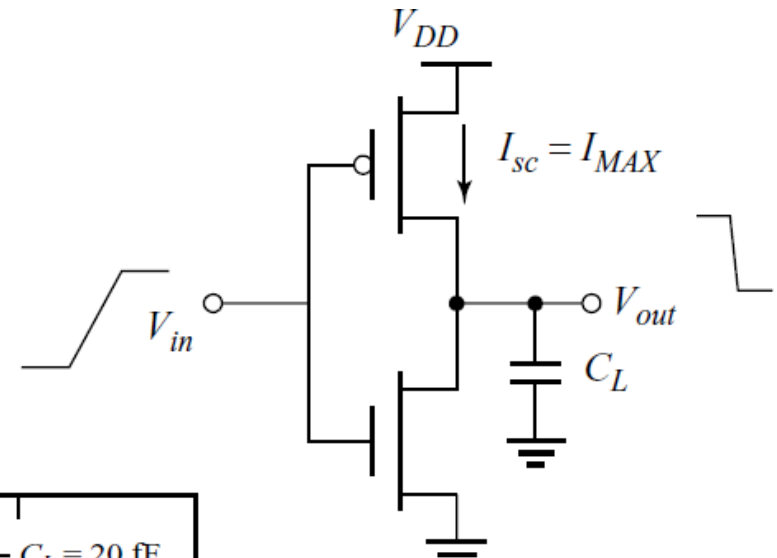**Pull-up turns off
before V_{Dsp} becomes
significant**



Small load

 


Best to maintain approximately equal input/output slopes

Leakage

- Leakage current of reverse biased S/D junctions
- Sub-threshold current of MOS devices
- no channel → **parasitic bipolar device**:
n+ (source) – p (bulk) – n+ (drain)
- Important source of leakage


 
$$I_D = I_0 e^{\frac{qV_{GS}}{nkT}} \left(1 - e^{-\frac{qV_{DS}}{kT}} \right) (1 + \lambda \cdot V_{DS})$$



Sub-Threshold Current

 


Figure 2


MOSFET current in both logarithmic (left) and linear (right) scales vs. gate voltage. The slope of the dotted line represents the large-signal transconductance for a digital circuit. Inset shows the band diagram of an n-MOSFET. The barrier height at $V_g = 0$ is proportional to V_t .

- Rapidly becomes bottleneck with lowering threshold voltages
- Modern technologies offer low- V_t and hi- V_t devices
Balance speed and power


Y. Taur, CMOS design near the limit of scaling, IBMJRD, Volume 46, Numbers 2/3, 2002

Sub-Threshold Current

 - Rapidly becomes bottleneck with lowering threshold voltages
- Modern technologies offer low- V_t and hi- V_t devices
Balance speed and power



Transistor Sizing for Minimum Energy

 

$$t_{pHL} \approx 0.52 \frac{C_L V_{DD}}{(W/L)_n k_n' V_{DSATn} (V_{DD} - V_{Tn} - V_{DSATn}/2)}$$

$$t_p = t_{p0} \left(\left(1 + \frac{f}{\gamma} \right) + \left(1 + \frac{F}{f\gamma} \right) \right)$$

$$t_{p0} \propto \frac{V_{DD}}{V_{DD} - V_{TE}}$$

See Eq. 5.21

$V_{TE} = V_T + \frac{1}{2}V_{DSAT}$: Effective V_T



Transistor Sizing (2)

$$t_p = t_{p0} \left(\left(1 + \frac{f}{\gamma} \right) + \left(1 + \frac{F}{f\gamma} \right) \right) \quad t_{p0} \propto \frac{V_{DD}}{V_{DD} - V_{TE}}$$

Performance Constraint (with $\gamma = 1$, $t_{pref} \rightarrow f=1$):


$$1 = \frac{t_p}{t_{pref}} = \frac{t_{p0}}{t_{p0ref}} \frac{\left(2 + f + \frac{F}{f} \right)}{(3 + F)} = \left(\frac{V_{DD}}{V_{ref}} \right) \left(\frac{V_{ref} - V_{TE}}{V_{DD} - V_{TE}} \right) \frac{\left(2 + f + \frac{F}{f} \right)}{(3 + F)}$$

- V_{TE} : technology (0.5 V), V_{ref} : standard supply (2.5 V)
- F: fanout
- V_{DD} , f: design parameters
- V_{DD} is a function of f, given a fixed performance

$$V_{DD} = \frac{f(15 + 5F)}{(14f - 8f^2 - 8F + 10fF)}$$

Transistor Sizing (3)

$$V_{DD} = f(f)$$

 

- Supply voltage needed as a function of f to maintain reference performance
- Lowest supply voltage needed for $f = F^{0.5}$

$$V_{DD} = \frac{f(15 + 5F)}{(14f - 8f^2 - 8F + 10fF)}$$

Transistor Sizing (4)

Energy for single Transition:

$$E = V_{DD}^2 C_{g1} [(1 + \gamma)(1 + f) + F]$$

$$\frac{E}{E_{ref}} = \left(\frac{V_{DD}}{V_{ref}} \right)^2 \left(\frac{2 + 2f + F}{4 + F} \right)$$

$C_{g1} + C_{int}$


Size of 1st +
2nd inverter

$C_L = FC_{G1}$

$$V_{DD} = \left(\frac{f(15 + 5F)}{14f - 8f^2 - 8F + 10fF} \right)$$

Transistor Sizing (5)

$$E/E_{ref} = f(f)$$

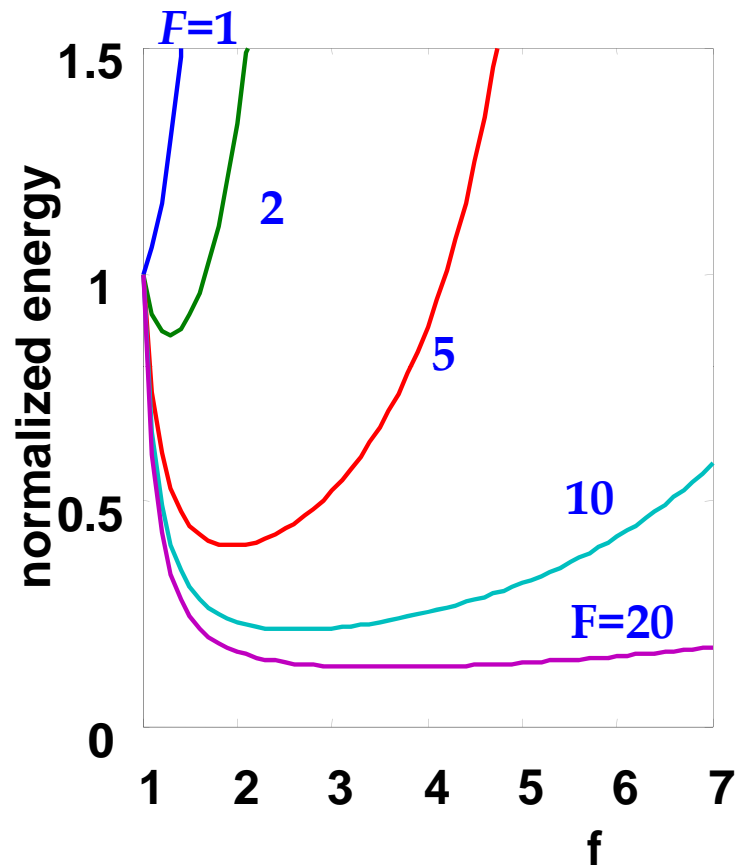

$$\frac{E}{E_{ref}} = \left(\frac{V_{DD}}{V_{ref}} \right)^2 \left(\frac{2 + 2f + F}{4 + F} \right)$$

- Device sizing is effective
- Oversizing is expensive for power
- Optimal sizing for energy slightly different from sizing for performance

Technology Scaling



Also see: IBM JRD, Vol 46, no 2/3, 2002

Scaling CMOS to the limit

<http://www.research.ibm.com/journal/rd46-23.html>




Moore's Law

  

The number of transistors that can be integrated on a single chip will double every 18 months

 Gordon Moore, co-founder of Intel
[Electronics, Vol 38, No. 8, 1965]



Why Scaling

- Reduce **price per function**:
 - Want to sell more functions (transistors) per chip for the same money → **better products**
 - Build same products cheaper, sell the same part for less money → **larger market**
 - Price of a transistor has to be reduced
- But also want to be **faster, smaller, lower power**




IC Technology Scaling

Scaling improves density and **performance**

■ First order **scaling theory**

■	dimensions,	$1/S$	<u>2008 / 1971</u>
■	voltages	$1/S$	0.007
■	intrinsic delay	$1/S$	0.007
■	power per transistor	$1/S^2$	0.00004

■ **Scaling trend**

   

first μ proc

Scaling Models

Fixed Voltage Scaling

- most common model until 1990's
- only dimensions scale, voltages remain constant

Full Scaling (Constant Electrical Field)

- ideal model — dimensions and voltage scale together by the same factor S

General Scaling

- most realistic for today's situation
- Two scaling factors:
 - dimensions scale with S
 - voltages scale with U

Scaling for Velocity Saturated Devices

Constant Field Scaling: $S = U$

Parameter	Relation	General Scaling
W, L, t_{ox}		$1/S$
V_{DD}, V_T		$1/U$
N_{SUB}	V / W_{depl}^2	S^2/U
Area / Device	WL	$1/S^2$
C_{ox}	$1/t_{ox}$	S
C_{gate}	$C_{ox} W L$	$1/S$
k_n, k_p	$C_{ox} W / L$	S
I_{sat}	$C_{ox} W V$	$1/U$
Current Density	$I_{sat} / Area$	S^2/U
R_{on}	V / I_{sat}	1
Intrinsic Delay	$R_{on} C_{gate}$	$1/S$
Power / Device	$I_{sat} V$	$1/U^2$
Power Density	$P / Area$	S^2/U^2

Technology Practice & ITRS

- **Scaling – Technology Generations**
- **$S \approx 1.4 \approx 2^{0.5}$ per generation**
- **... – 250 – 180 – 130 – 90 – 65 – 45 – 35 – 22 – ... nm**

- **ITRS: International Technology Roadmap for Semiconductors**
Industry-wide organization for forecasting technology developments – and (planning) requirements




<http://www.itrs.net/home.html>



**Not really – it is more like science
(and a self-fulfilling prophecy at the same time)**




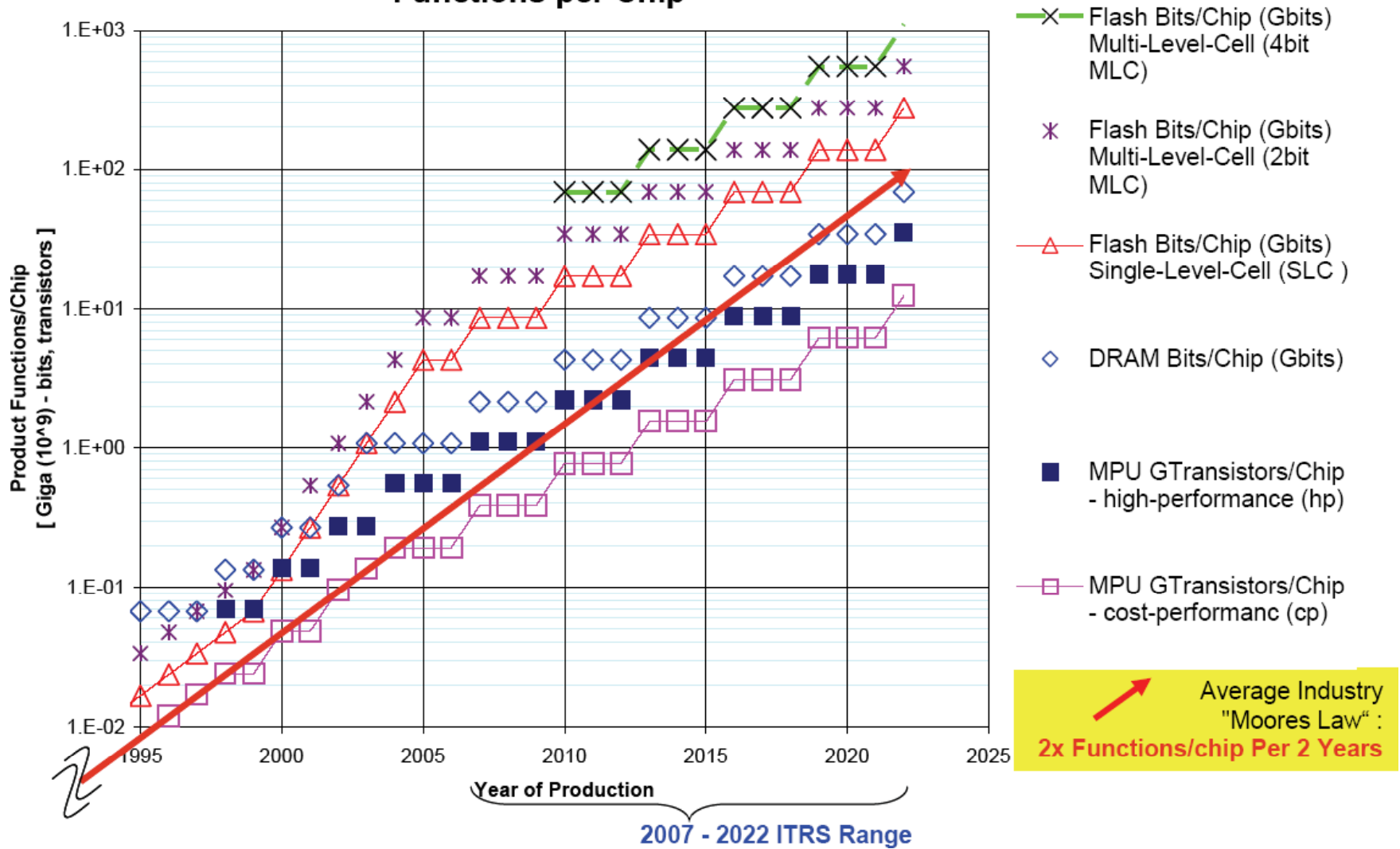2007 ITRS Product Technology Trends - Functions per Chip





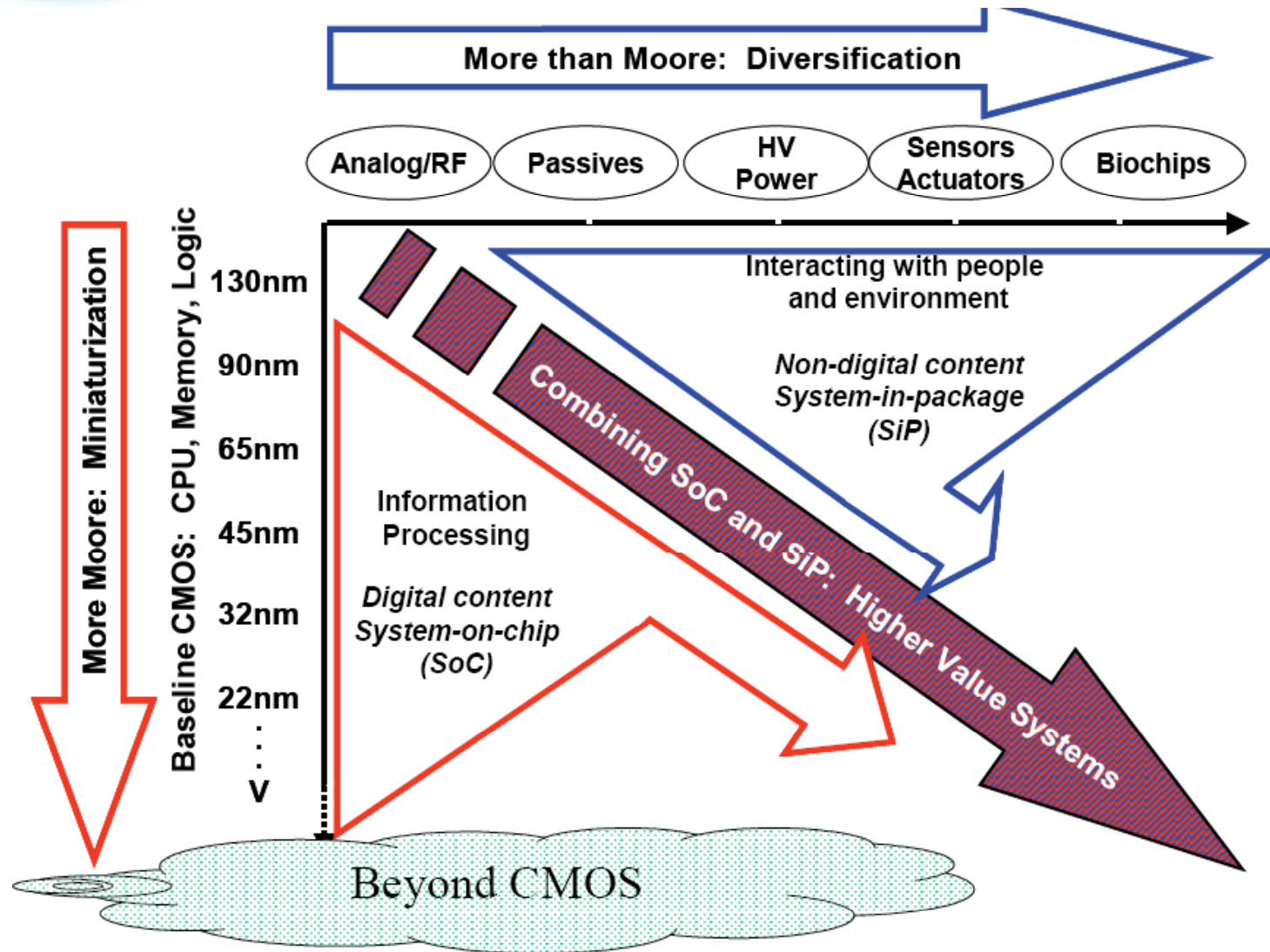International Technology Roadmap for Semiconductors



Summary

- **Digital Gate Characterization (§ 1.3)**
- **Static Behavior (Robustness) (§ 5.3)**
 - **VTC**
 - **Switching Threshold**
 - **Noise Margins**
- **Dynamic Behavior (Performance) (§ 5.4)**
 - **Capacitances**
 - **Delay**
- **Power (§ 5.5)**
 - **Dynamic Power, Static Power, Metrics**
- **Scaling (§ 5.6)**