

MODULE 7

MODULARITY

Outline

- **Background on Modular Design**
 - **Hierarchy, reuse, regularity**
 - **Architecture, bit-slicing**
- **Adder Design**
- **(Multiplier Design)**
- **Shifter Design**
- **Layout Strategies (regularity)**
- **Design as a Trade-Off**


**contains a lot
of reminders**

**Get further appreciation of some
system level design issues**

Anonymous Transistors

- Large Chips have $> 10^8$ transistors
- Cannot consider each transistor separately during design
- Large chips have many “anonymous transistors” [Chris Verhoeven]
- Assembled from pre-designed building blocks
 - Such as on chip memory blocks
 - Or other blocks ranging from adders to complete sub systems [e.g. MP3 decoder, memory, ...]
- Blocks are assembled from sub blocks, and so on
- Block types depend on architecture

Design Levels

 

7 - timing design

8 - modularity

6 - sequential



5 - combinational

4 - inverter

2 - devices

3 - process


Hierarchy - Modularity

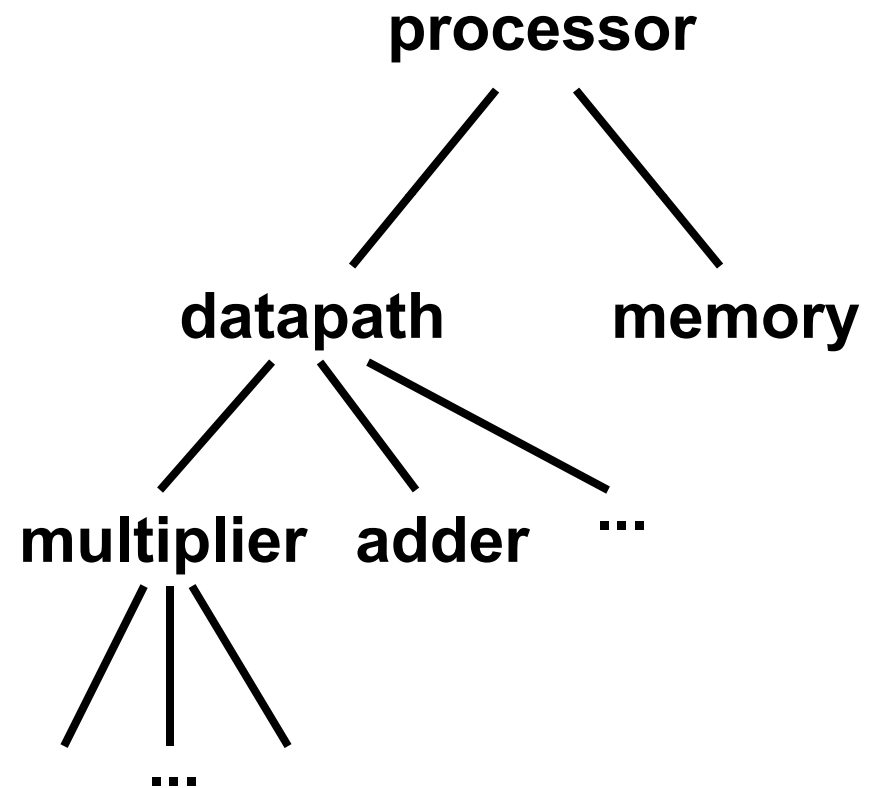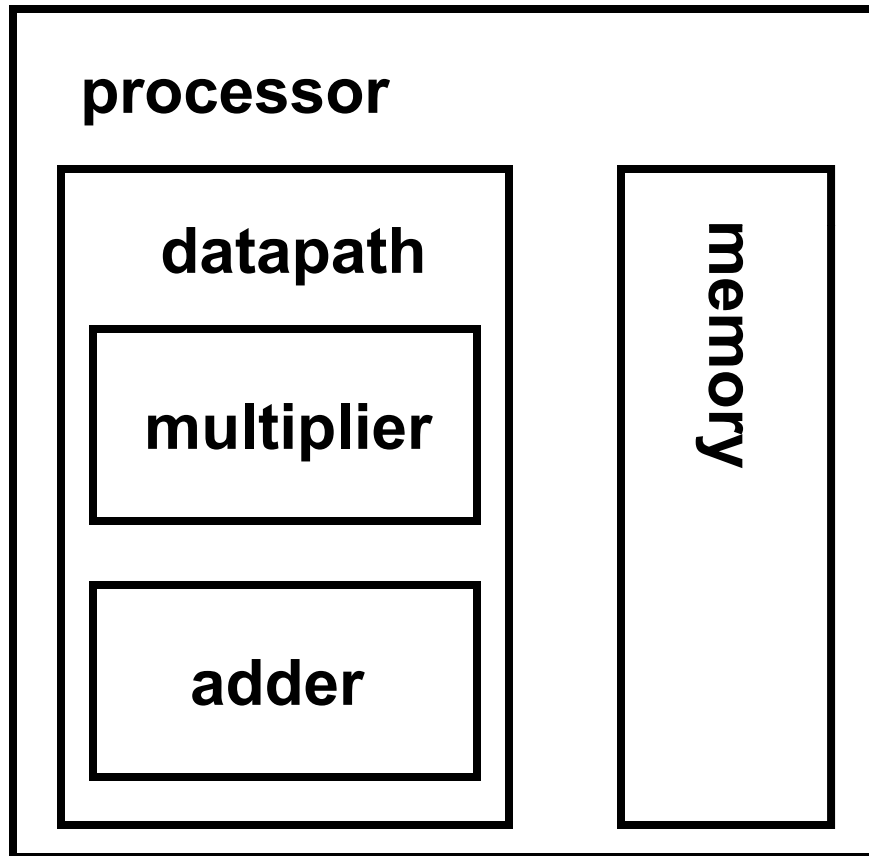


Modularity - Regularity

- **Regularity at architecture level**
 - **At logic level**
 - **At transistor level**
 - **At layout level**
-
- **Bit-slices, abutment, array-structures,**

A Generic Digital Processor

 


Itanium Datapath Pipeline

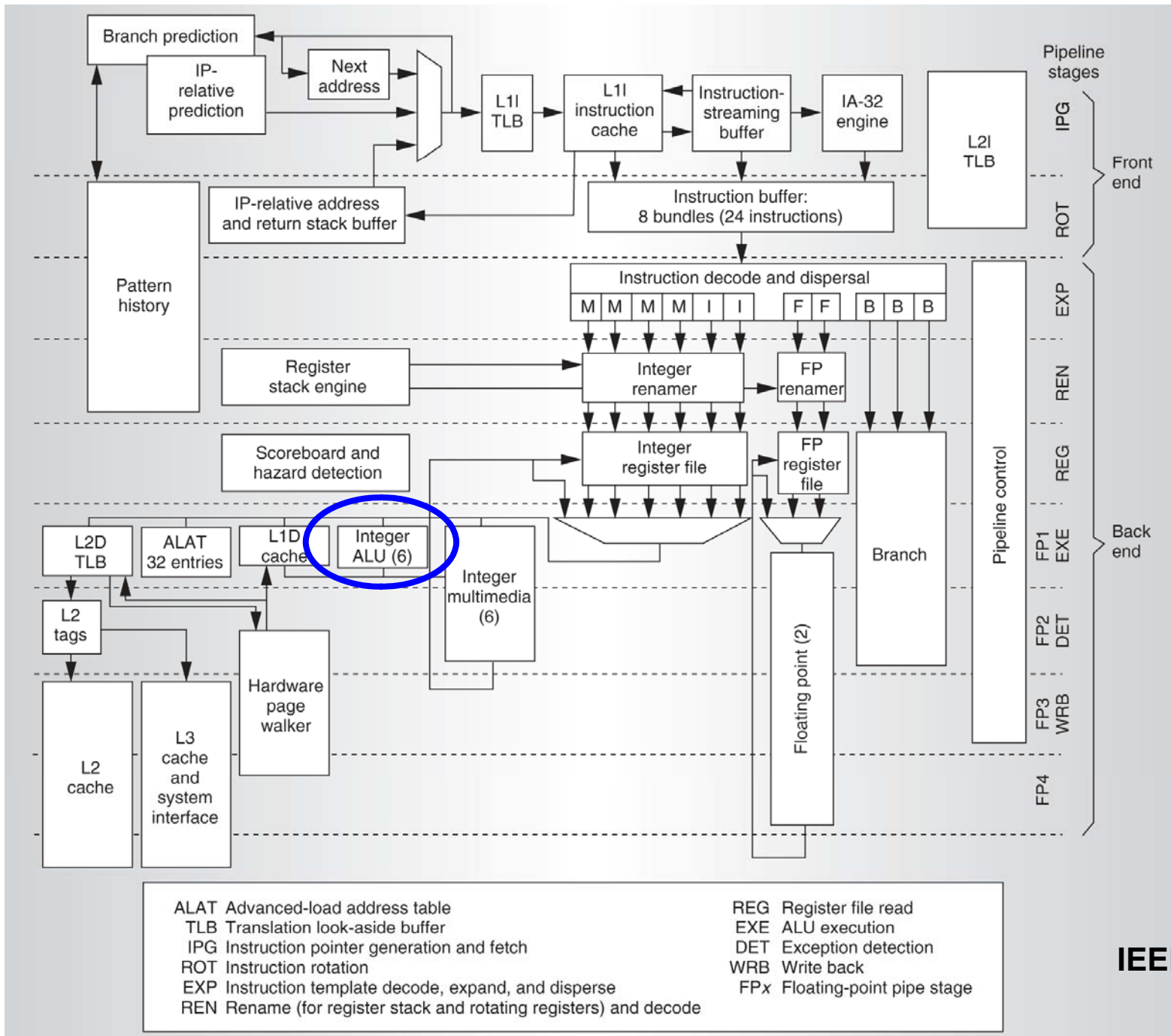


McNairy
IEEE Micro 2003

Itanium Integer Unit

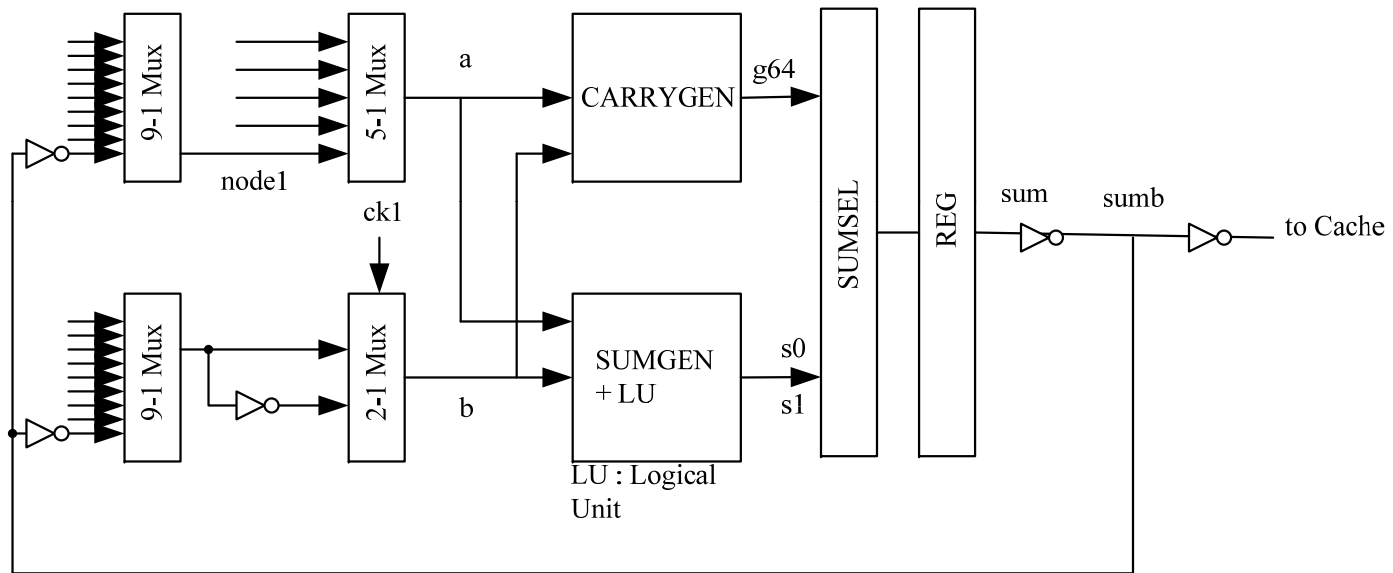


Itanium has 6 integer execution units like this

Itanium Integer Datapath

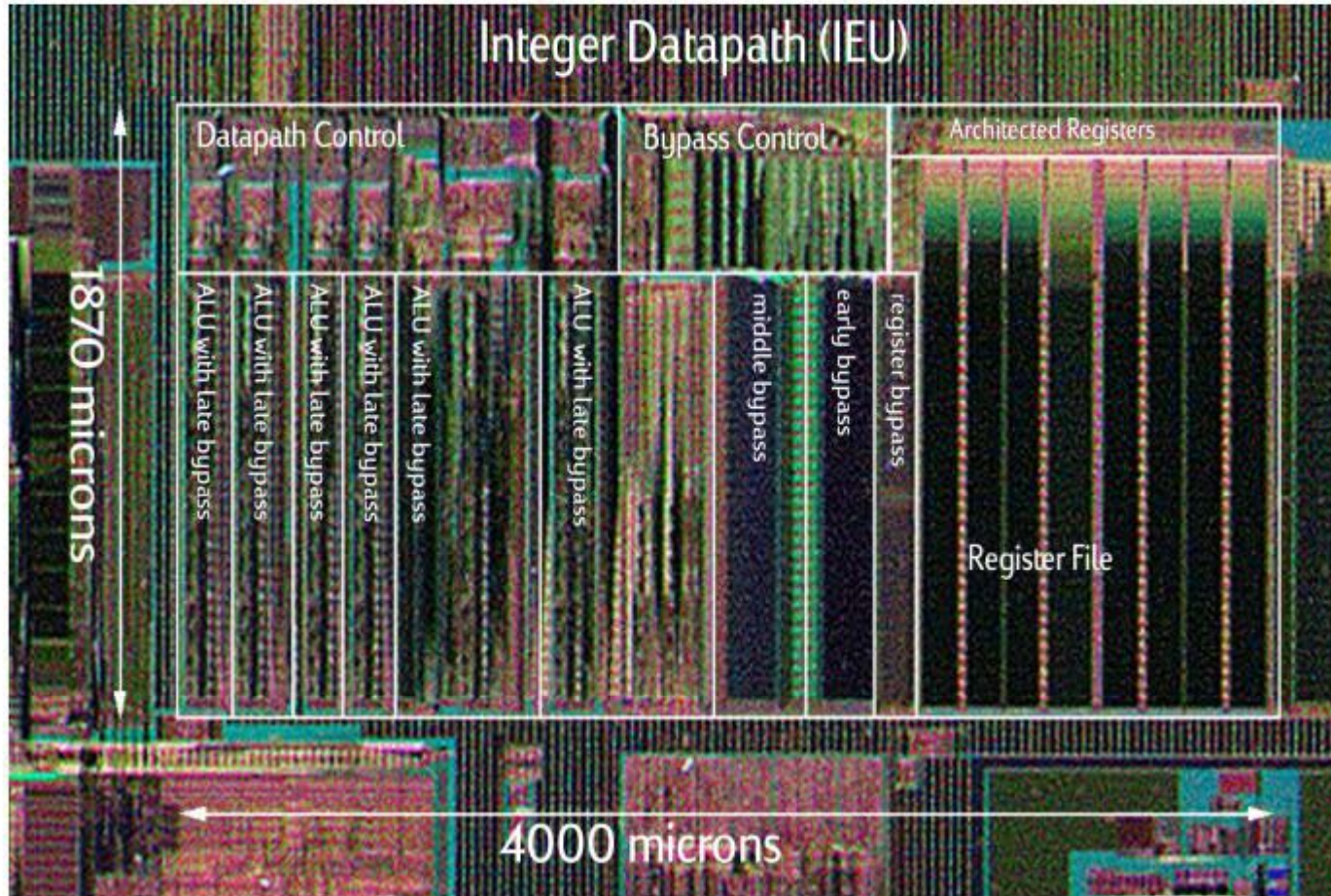


Fetzer, Orton, ISSCC'02

Bit-Sliced Design

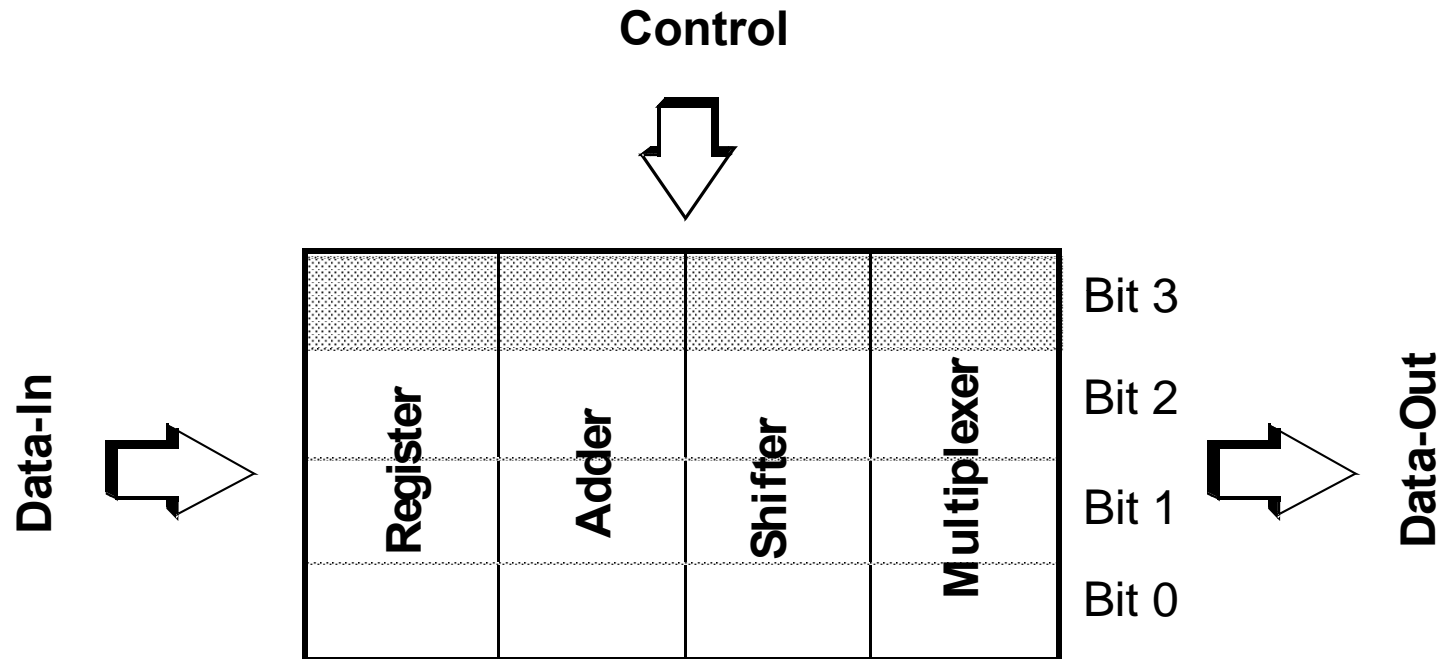

Tile identical processing elements

Bit-Sliced Datapath

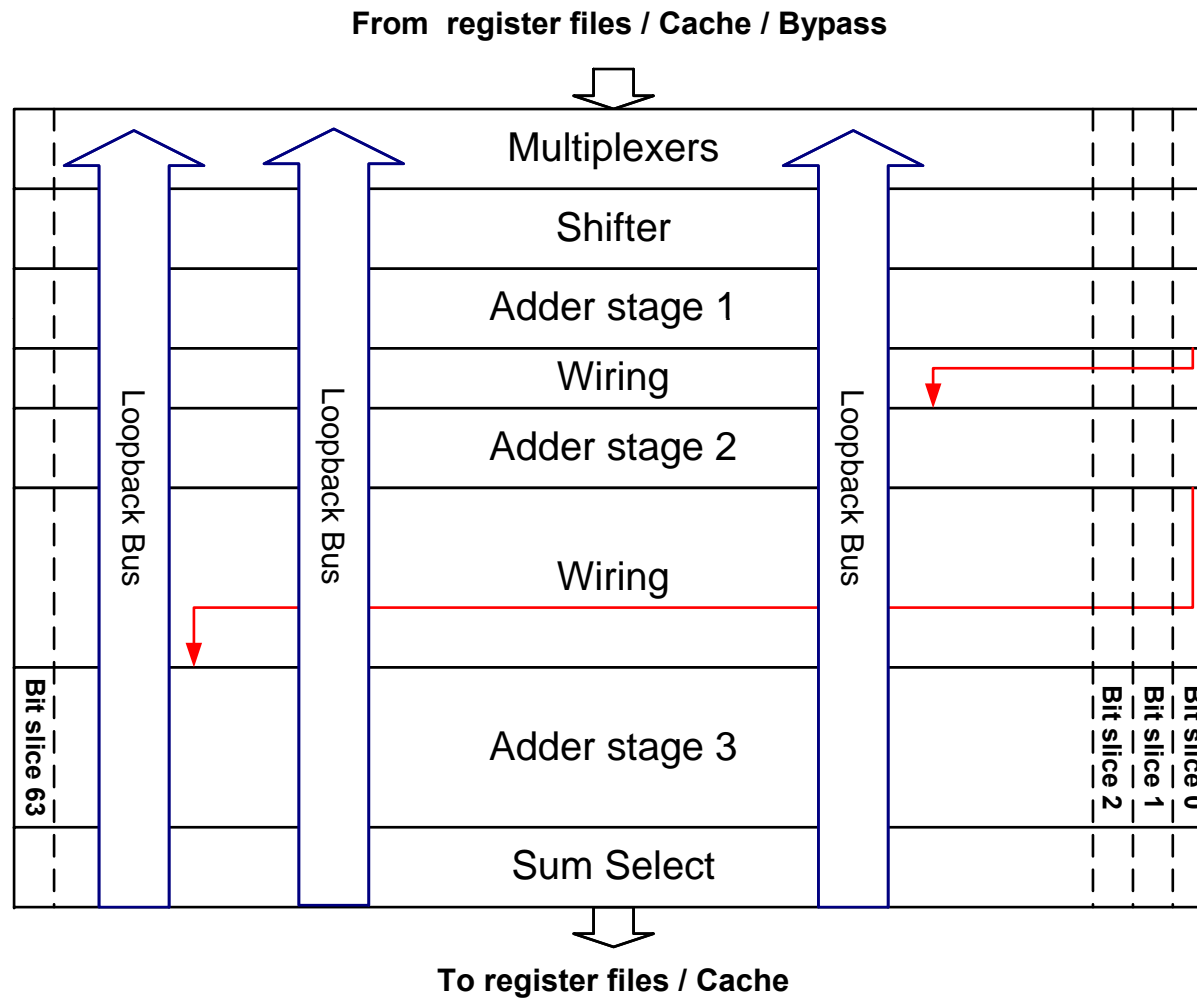

Building Blocks for Digital Architectures

✓ Arithmetic unit

- Bit-sliced datapath (**adder**, multiplier, shifter, comparator, etc.)

✗ Memory

- RAM, ROM, Buffers, Shift registers

✗ Control


- Finite state machine (PLA, random logic.)
- Counters

✗ Input-Output

- Off-chip drivers, receivers

✗ Interconnect

- Switches
- Arbiters
- Bus

 


Adder Design

- Adders are fundamental building blocks
 - Digital filtering (DSP): MP3 en/decoder, GSM, GPS, ...
 - Data processing
 - Multiplication
 - Address arithmetic
 - ...
 - Good performance is key
 - Many architectures
 - Static adder
 - Dynamic adder (Manchester Carry Chain)
 - Pipelined Adder
 - Carry-Bypass, Carry Lookahead, Carry Select
 - ...
 - Design trade-offs, optimization
 - Architecture level
 - Logic level
 - Circuit level
 - Layout level
- ↑ Most effective
↓ Least effective



Full-Adder

 


Add three one-bit numbers

Equivalently: count # 1's in A, B, C_i


Output as 2-bit number <C_{out} S>

C _{in}	B	A	C _{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

The Ripple-Carry Adder

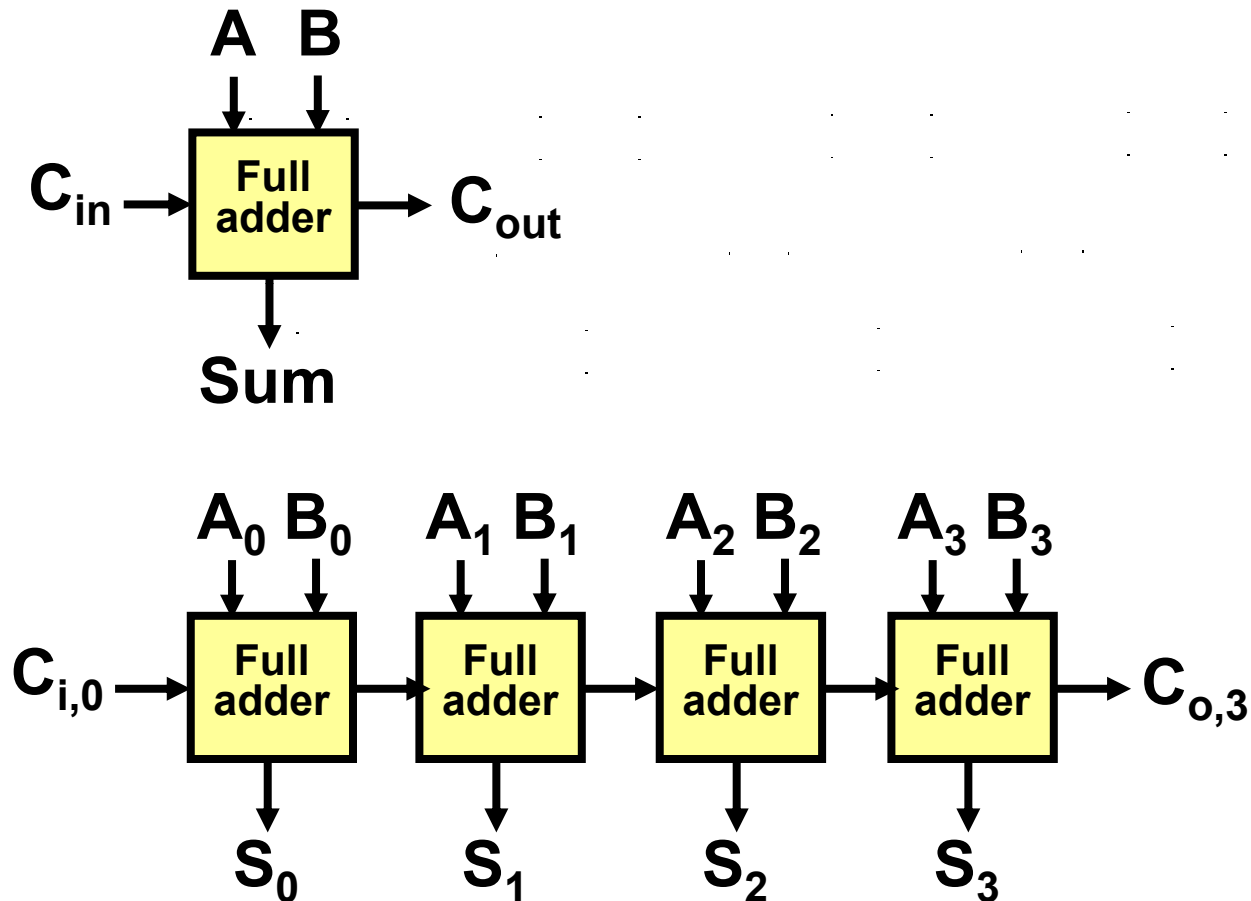

The Binary Adder

 

	\bar{c}	c
$\bar{a}\bar{b}$		1
$\bar{a}b$	1	
ab		1
$a\bar{b}$	1	

(a) SUM

	\bar{c}	c
$\bar{a}\bar{b}$		
$\bar{a}b$		1
ab	1	1
$a\bar{b}$		1


(b) CARRY

$AB + BC + AC$

$$\begin{aligned}
 S &= A \oplus B \oplus C_i \\
 &= \bar{A}\bar{B}C_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i \\
 C_0 &= AB + BC_i + AC_i
 \end{aligned}$$

AND-OR expressions for sum and carry

Full Adder Logic

 

$$S = A \oplus B \oplus C_i$$
$$C_o = AB + BC_i + AC_i = AB + (A \oplus B) C_i$$

Why is this not so good in CMOS?

Naive Complementary CMOS Implementation


- Use DeMorgan to convert AND-OR expressions for *SUM* and *CARRY* to NAND-NAND

- $PQ + RS = \overline{\overline{PQ} \overline{RS}}$ (example)

Transistor Count


- 3 × INVERT
- 3 × NAND-2
- 5 × NAND-3
- 1 × NAND-4

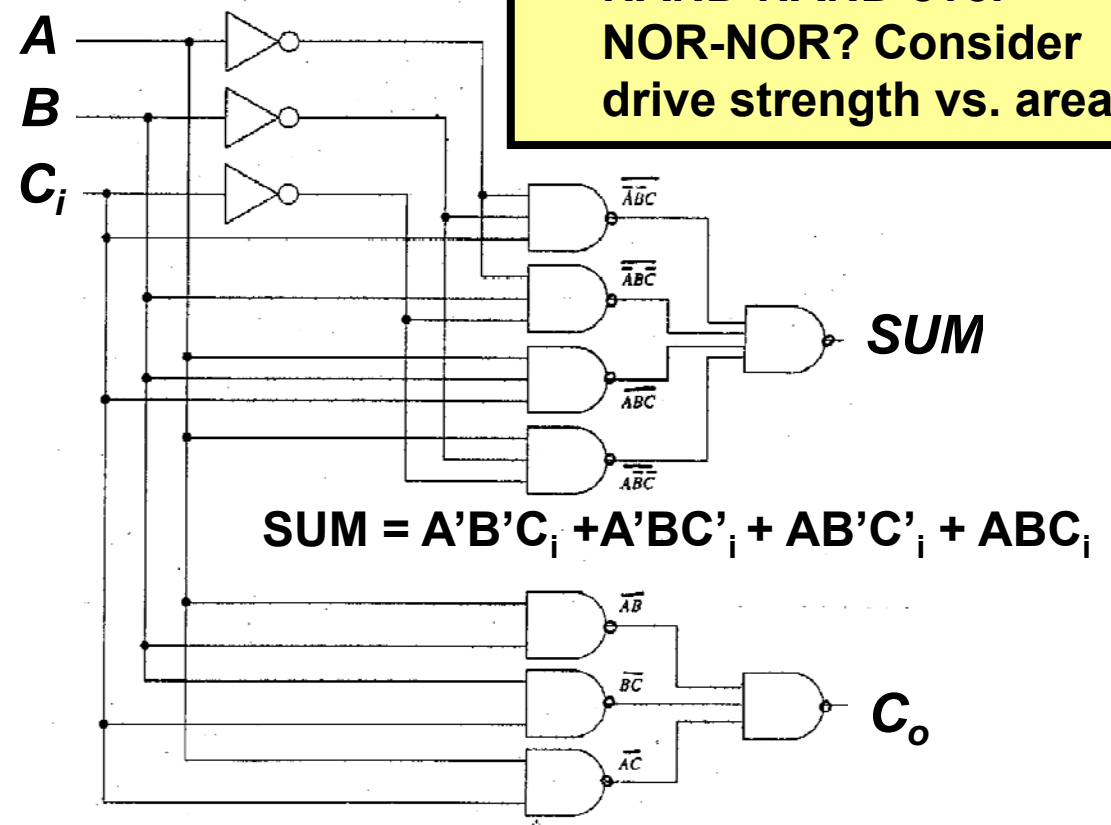Q: What is advantage of NAND-NAND over NOR-NOR? Consider drive strength vs. area



Can do better using more clever boolean factoring, but...

Nand/Nand vs Nor/Nor

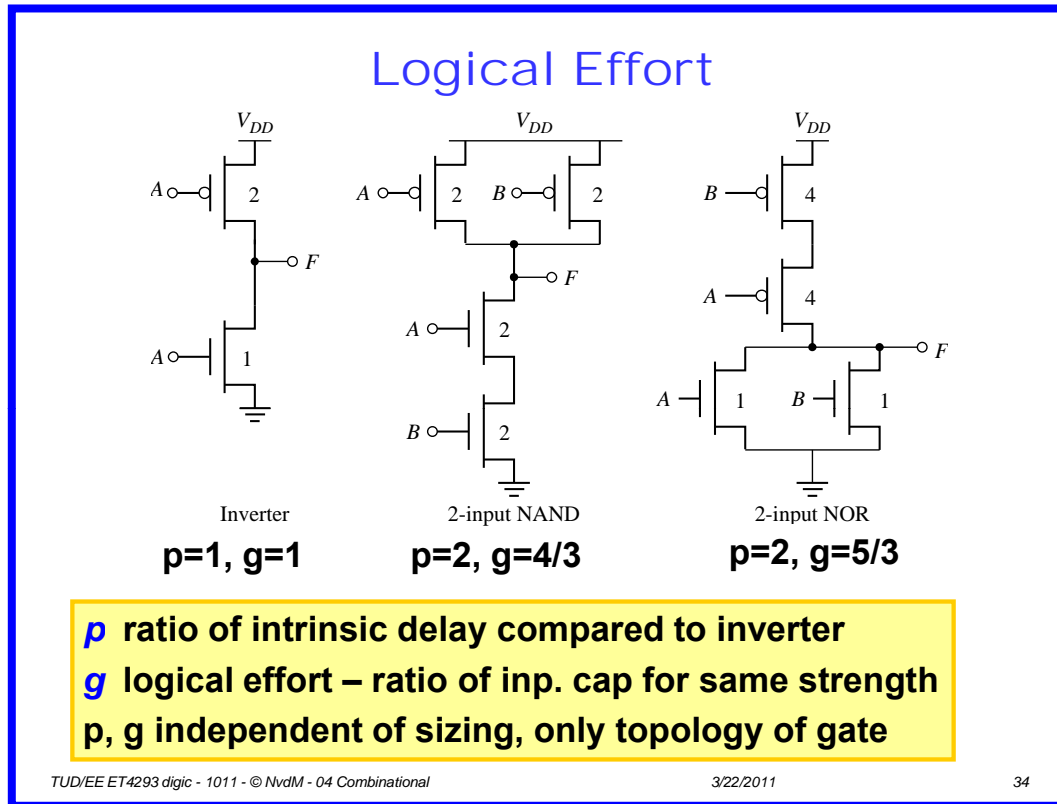

NAND Logical Effort: $(n+2)/3$

NOR Logical Effort: $(2n+1)/3$


Full-Adder Boolean Factoring

$$\begin{aligned} S &= \bar{A}\bar{B}\bar{C}_i + \bar{A}B\bar{C}_i + A\bar{B}\bar{C}_i + ABC_i \\ &= ABC_i + \bar{C}_0(A + B + C_i) \end{aligned}$$

$$\begin{aligned} C_0 &= AB + BC_i + AC_i \\ &= AB + (A + B)C_i \end{aligned}$$

C_{in}	B	A	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Improved Complementary Static Full Adder

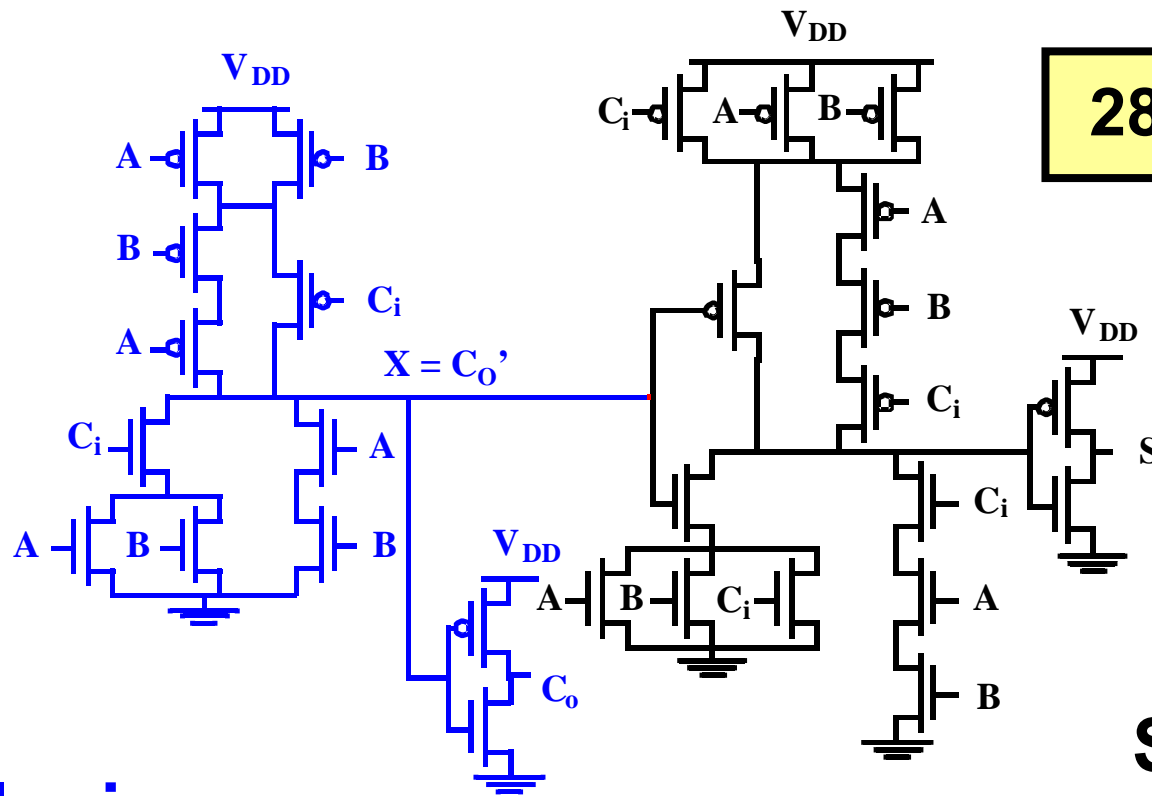

28 Transistors


Carry logic

$$C_0 = AB + (A + B)C_i$$

Sum logic


$$S = ABC_i + \bar{C}_0(A + B + C_i)$$

Ripple-Carry Adder Delay

 

- Worst case delay through full carry path (ripple carry)
- Linear with the number of bits (N)
- $T_{\text{adder}} = (N-1) T_{\text{carry}} + \text{Max} (T_{\text{carry}}, T_{\text{sum}})$
- $T_{\text{adder}} = O(N)$ “ T_{adder} is of Order N” *means linear with N*
- **Goal: Make the fastest possible carry path circuit**


Adder Evaluation

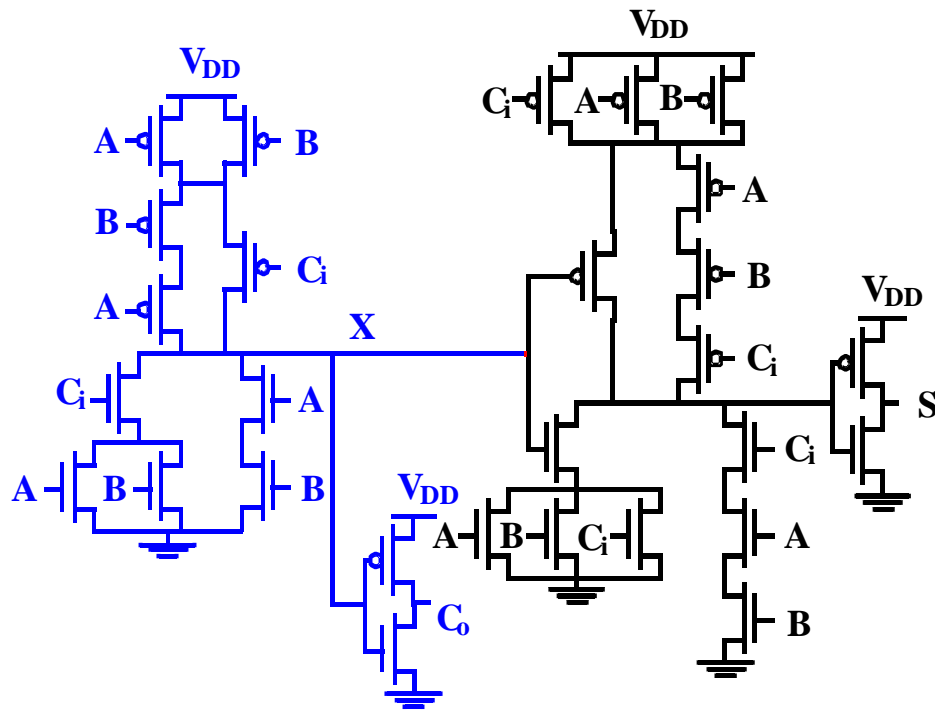

Carry Chain:

- Long PMOS chains
- High C at X
- 2 (inverting) stages

Inversion Property

 


C_{in}	B	A	C_{out}	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Mirror Symmetry

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$


$$\bar{C}_0(A, B, C_i) = C_0(\bar{A}, \bar{B}, \bar{C}_i)$$

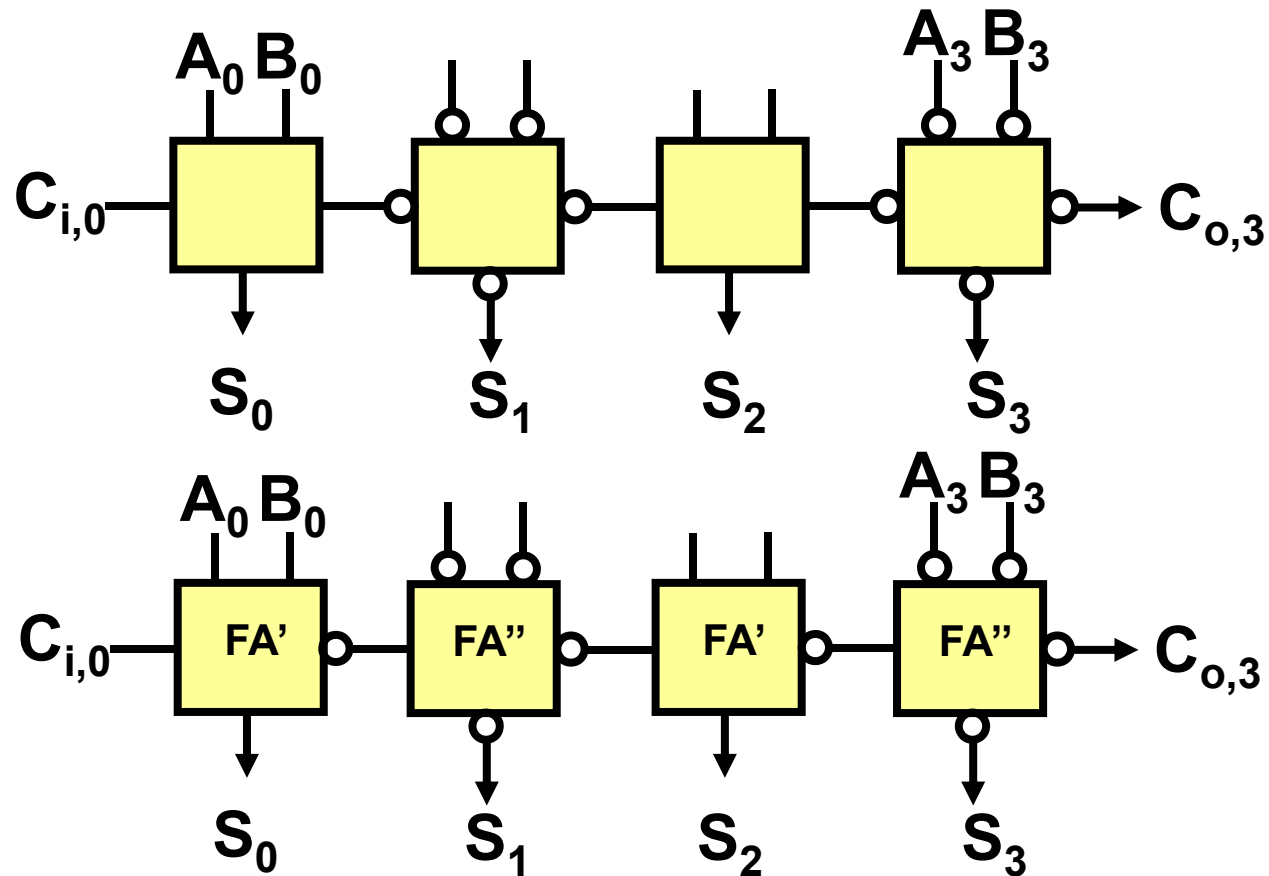Minimize Critical Path by Reducing Inverting Stages



- Can eliminate inverter in carry from each FA
- Need 2 different types of cells, but both with inverting carry – will require only one stage per bit

Eliminate Inverter In Carry.

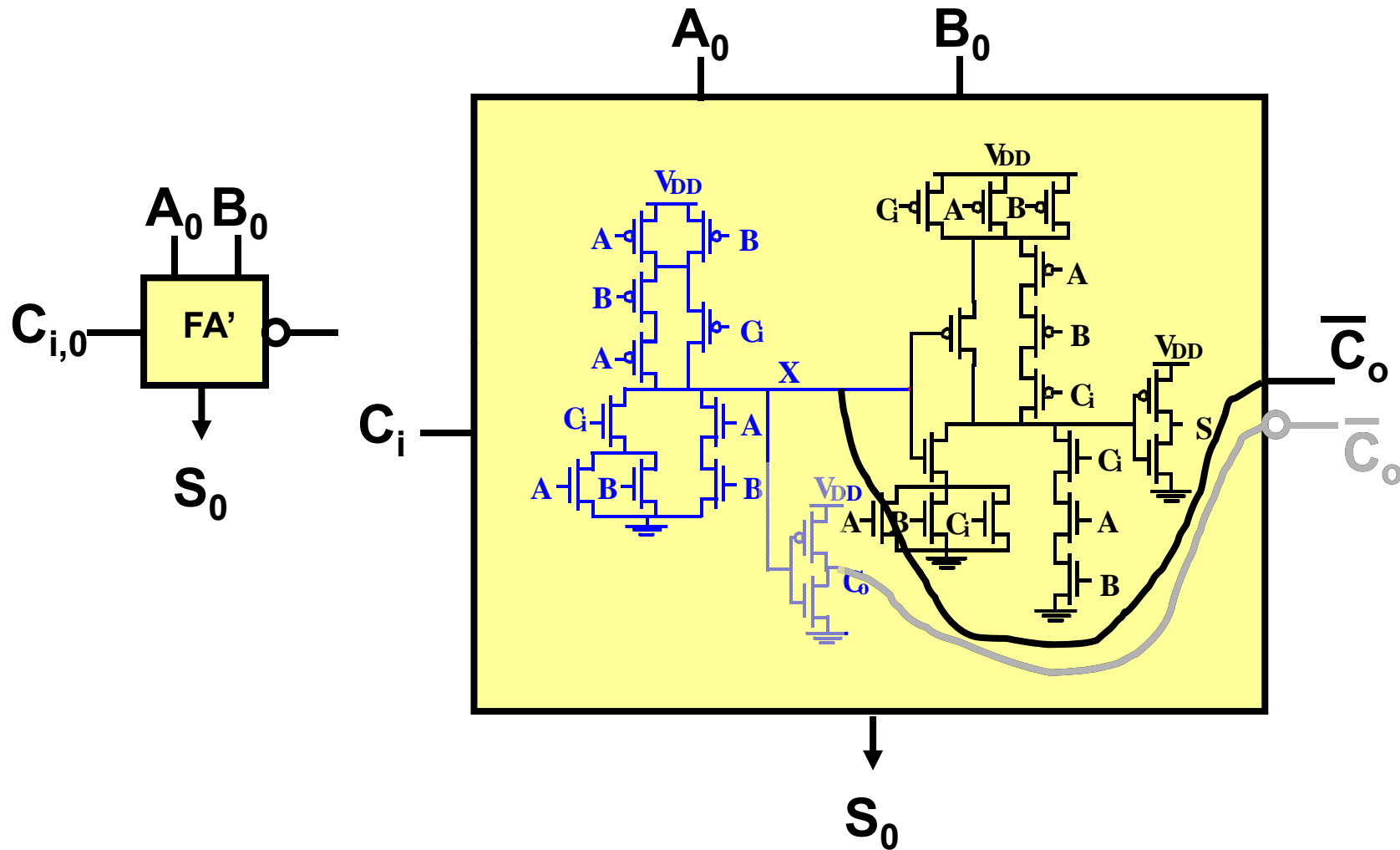

Further Boolean Factoring

- **Goal: fastest carry computation possible**
- **Pre-compute intermediate variables based on A, B, and when C_i arrives, C_o is almost ready**
- **The intermediate variables are called**
 - P (Propagate)**
 - G (Generate)**
 - K (Kill) aka D (Delete)**
- **Only one or two of these are needed**


Carry Status Intermediate Variables

A	B	C_i	S	C_o	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

$\overline{A}\overline{B}$

$A \oplus B$

AB


 


- P, G, D **ONLY** depend on A, B
- Simple and fast expressions for S and C_o based on G, P and C_i
- Or D instead of G

$$C_o (G, P) = G + PC_i$$


$$S (G, P) = P \oplus C_i$$

Carry – Dual PU/PD vs Mirror Structure

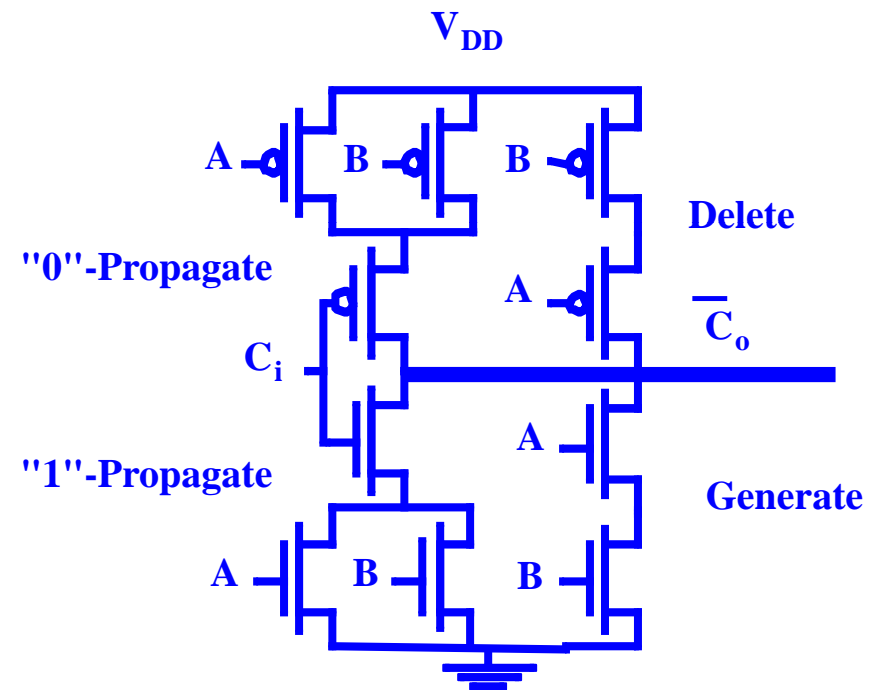 

Mirror Adder - Carry Logic


A	B	C_i	S	C_o	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

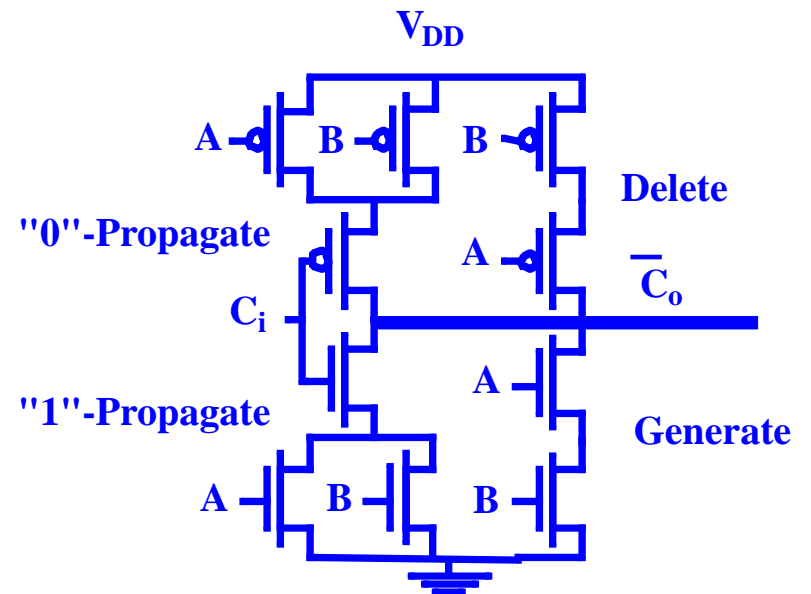


$$C_o (G, P) = G + PC_i$$

$$S (G, P) = P \oplus C_i$$

Mirror Adder - Symmetrical Sum Logic

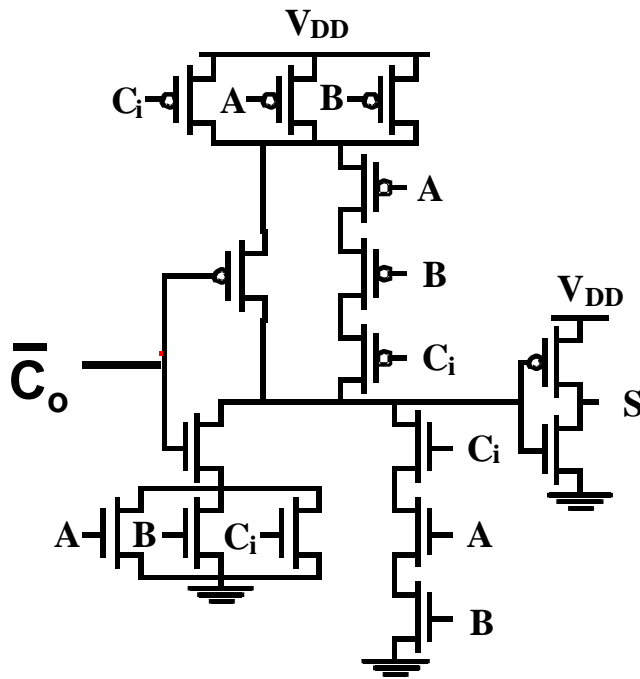


Dual Structure

 

Symmetrical Structure


Mirror Adder - Symmetrical Sum Logic

A	B	C_i	S	C_o	Carry status
0	0	0	0	0	delete
0	0	1	1	0	delete
0	1	0	1	0	propagate
0	1	1	0	1	propagate
1	0	0	1	0	propagate
1	0	1	0	1	propagate
1	1	0	0	1	generate
1	1	1	1	1	generate

 

- No need to restrict topologies to strictly dual
- But must always obey **Mutual Exclusion Principle** (and in static CMOS, output must always be driven)


Mirror Adder – Complete.

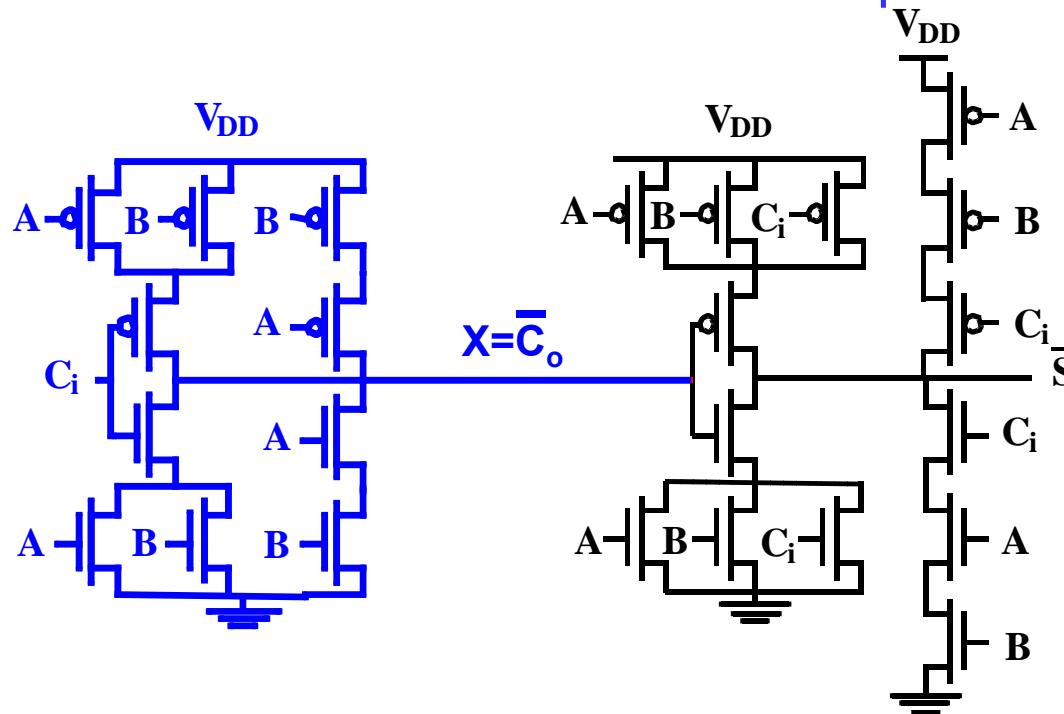


- Symmetrical NMOS/PMOS chains ==> **symmetrical timing**
- **Max 2 PMOS in series** in carry chain
- High capacitance at X, but **only one stage in carry**
... and can optimize layout to reduce (diffusion) cap at X
- Transistors connected to **C_i** closest to output
- **Only** transistors in **carry chain need size optimization** for speed
rest can be minimum size

Mirror Adder


Stick Diagram

 


Transmission Gate Full Adder

 

Setup

 

(Propagate) $P = A \oplus B$

 

Sum Generation

Carry Generation

(Generate) $G = AB$


(Propagate) $P = A \oplus B$

(Delete) $D = \bar{A} \bar{B}$


$$C_o (G, P) = G + PC_i$$

$$S (G, P) = P \oplus C_i$$


Manchester Carry Chain

 

Manchester Carry Chain

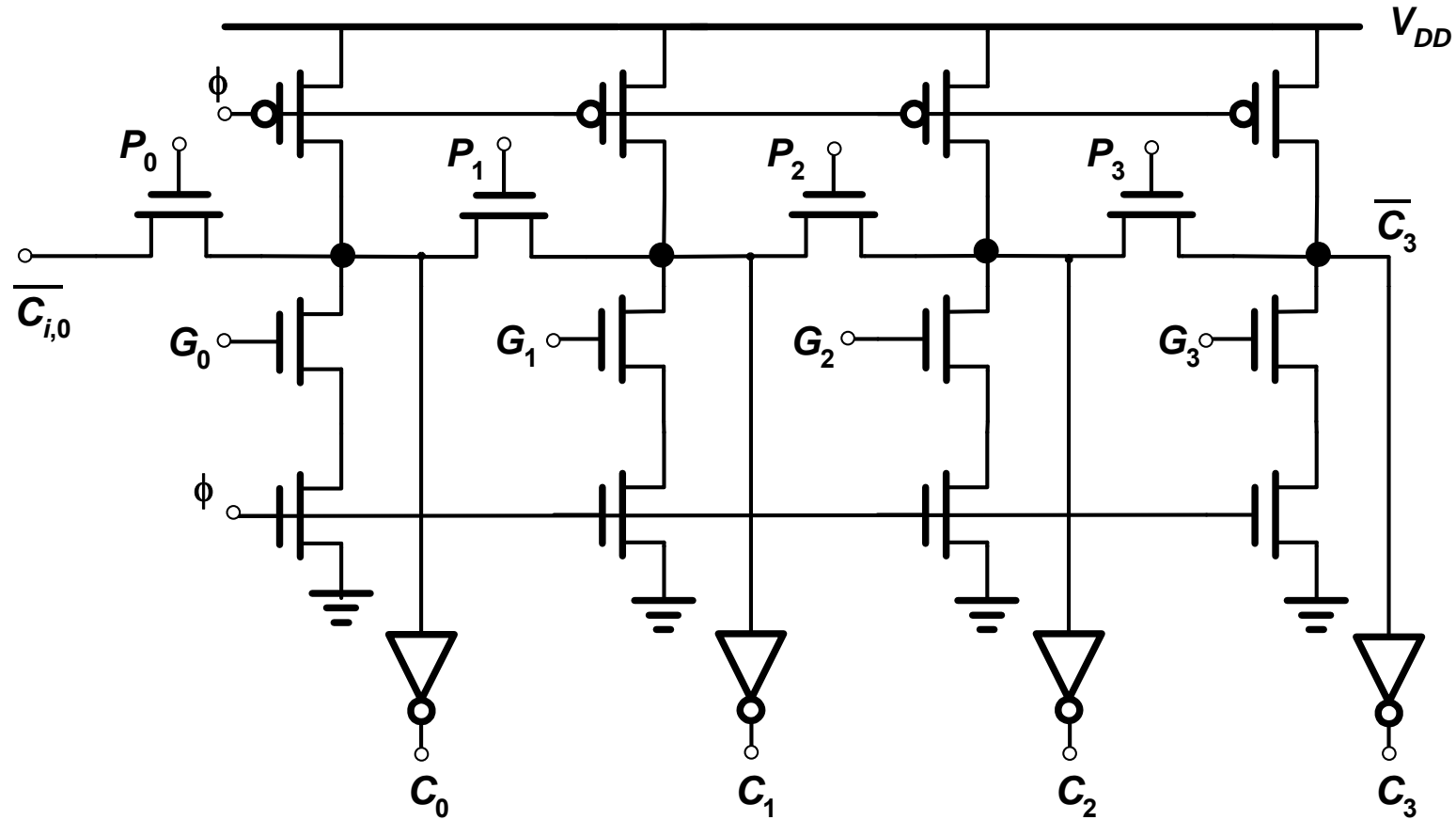


Manchester Carry Chain Delay

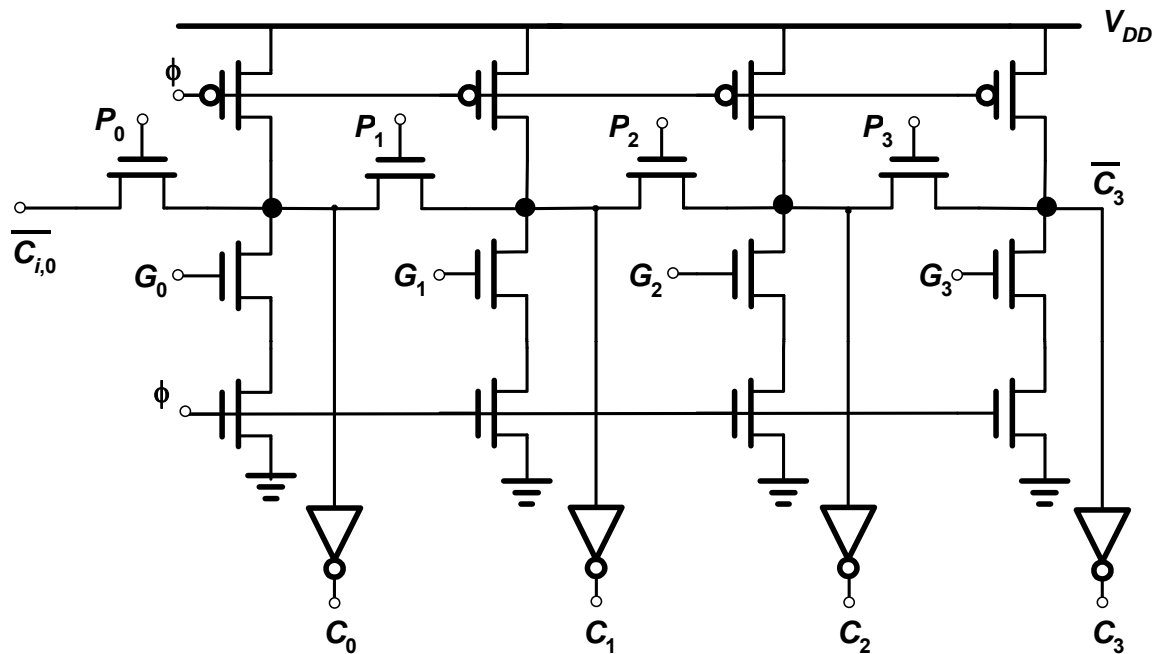


**Given an expression of delay (symbols, not numbers)
as a function of the number of bits**

Manchester Carry Chain

Stick Diagram

 


Carry-Bypass Adder

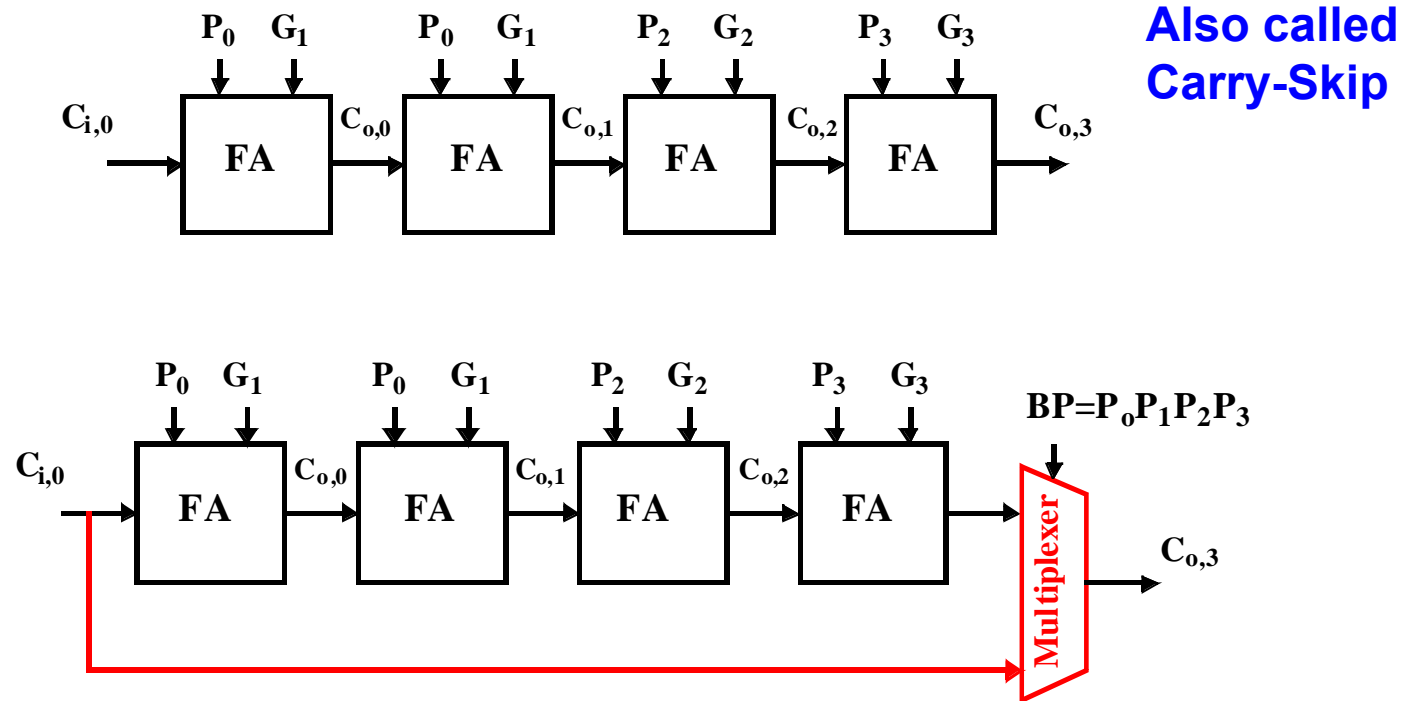


Idea: If (P_0 and P_1 and P_2 and $P_3 = 1$)
then $C_{o3} = C_0$, else “kill” or “generate”.

Carry-Bypass Adder (cont.)

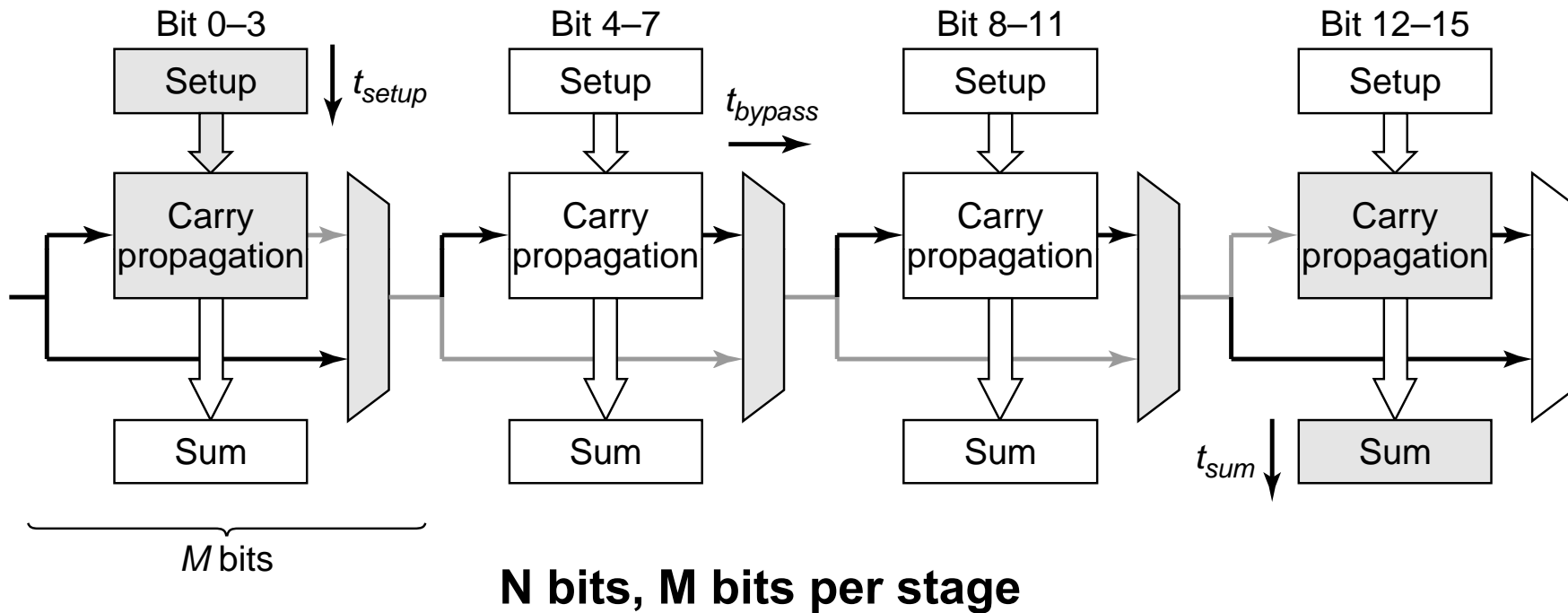


$$t_{adder} = t_{setup} + M t_{carry} + (N/M - 1) t_{bypass} + (M - 1) t_{carry} + t_{sum}$$


Carry Ripple versus Carry Bypass

 

Carry-Select Adder

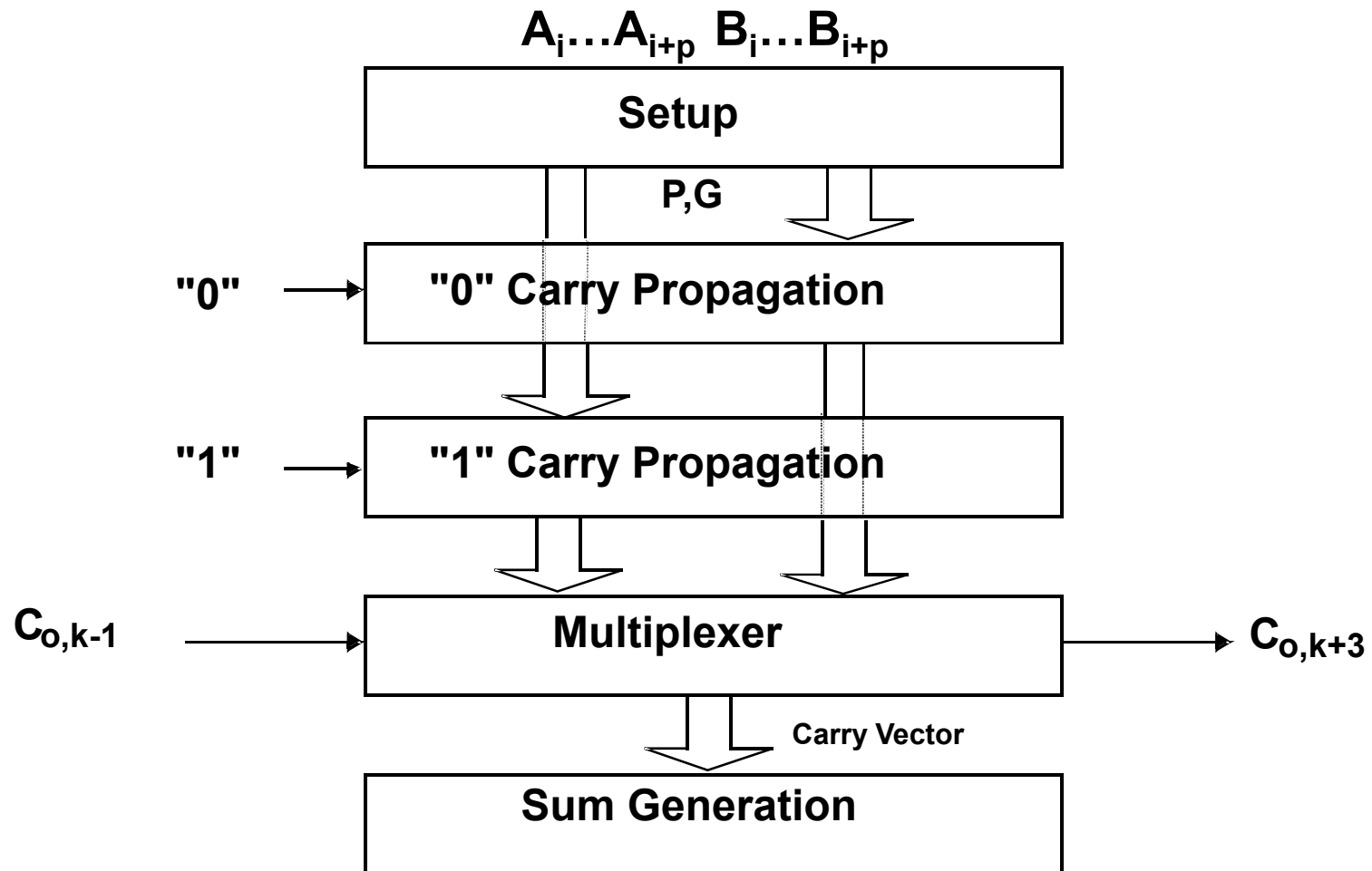

Carry Select Adder: Critical Path

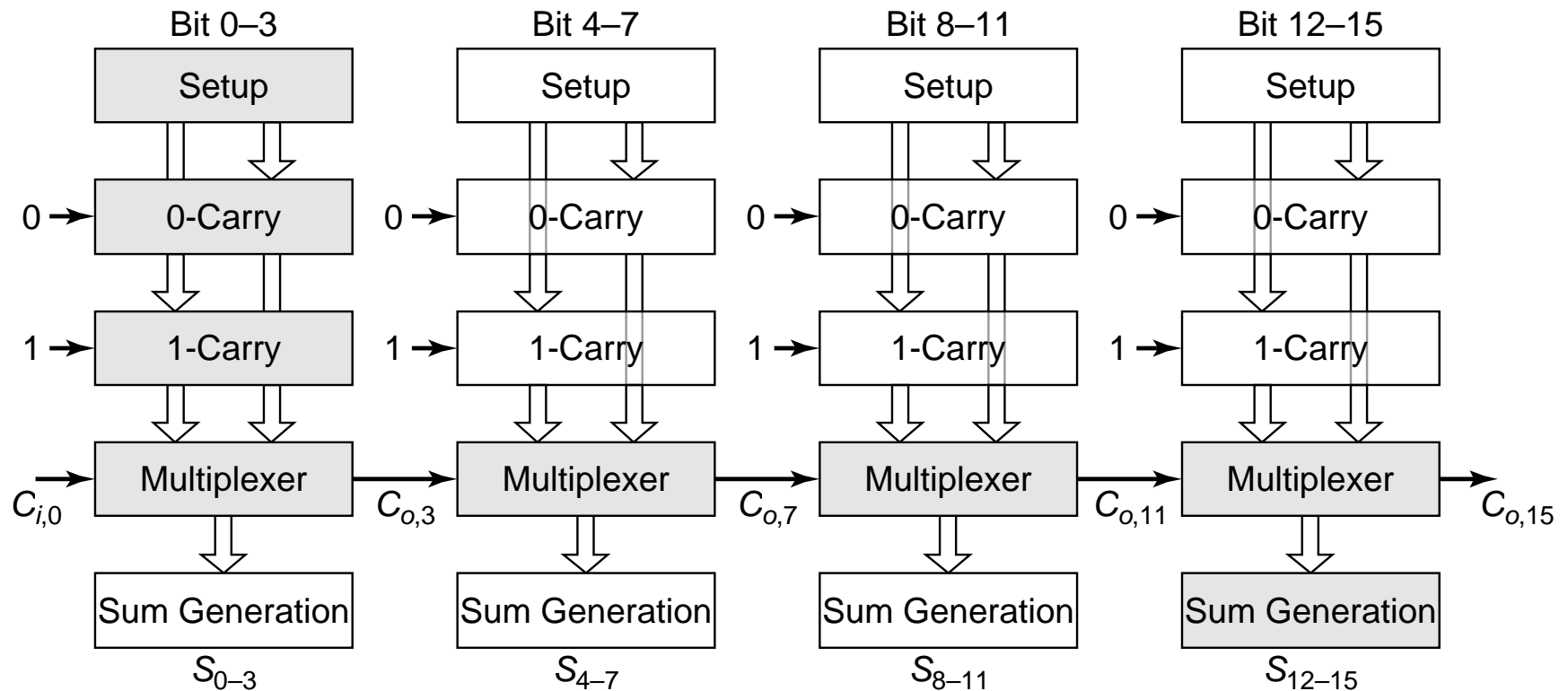


N bits, M bits/stage

t_{carry} is delay per bit

$$t_{\text{add}} = t_{\text{setup}} + Mt_{\text{carry}} + \left(\frac{N}{M}\right)t_{\text{mux}} + t_{\text{sum}}$$

Linear Carry Select

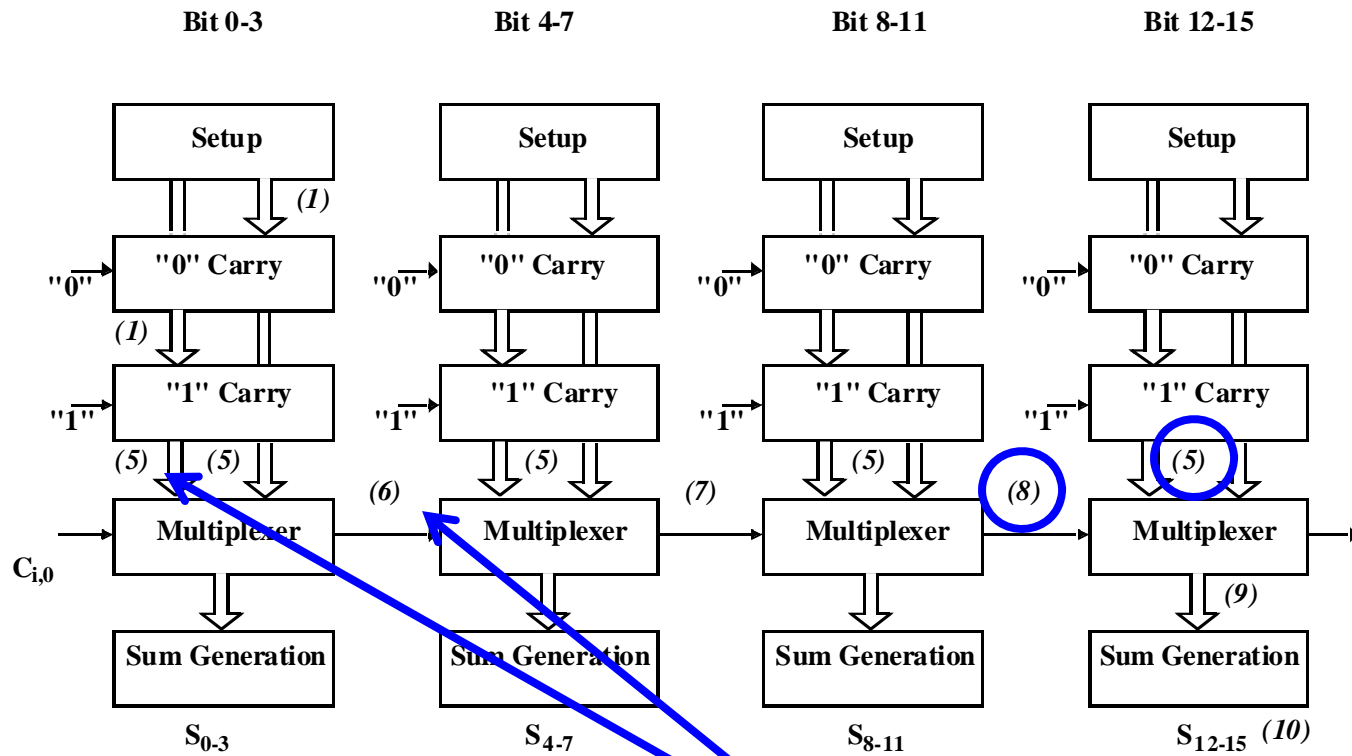


Assume unit delays per block, delays annotated as such

There is some slack

Square Root Carry Select

P stages of increasing width

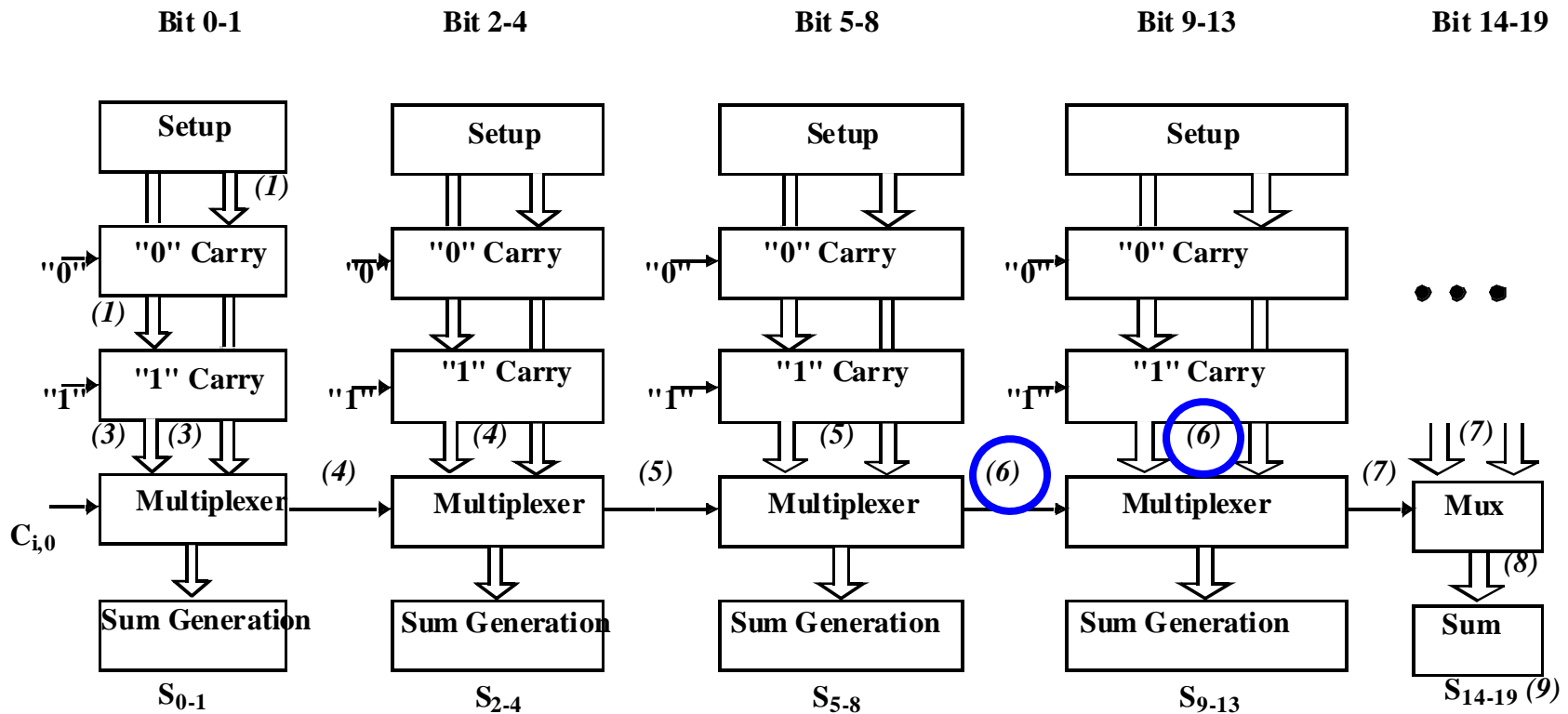


$$N = M + (M + 1) + (M + 2) + \dots + (M + P - 1)$$

$$= MP + \frac{P(P-1)}{2} = \frac{P^2}{2} + P\left(M - \frac{1}{2}\right) \approx \frac{P^2}{2} \quad \text{if } N \gg M$$

$$P = \sqrt{2N} \Rightarrow$$

$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$

Adder Delays - Comparison

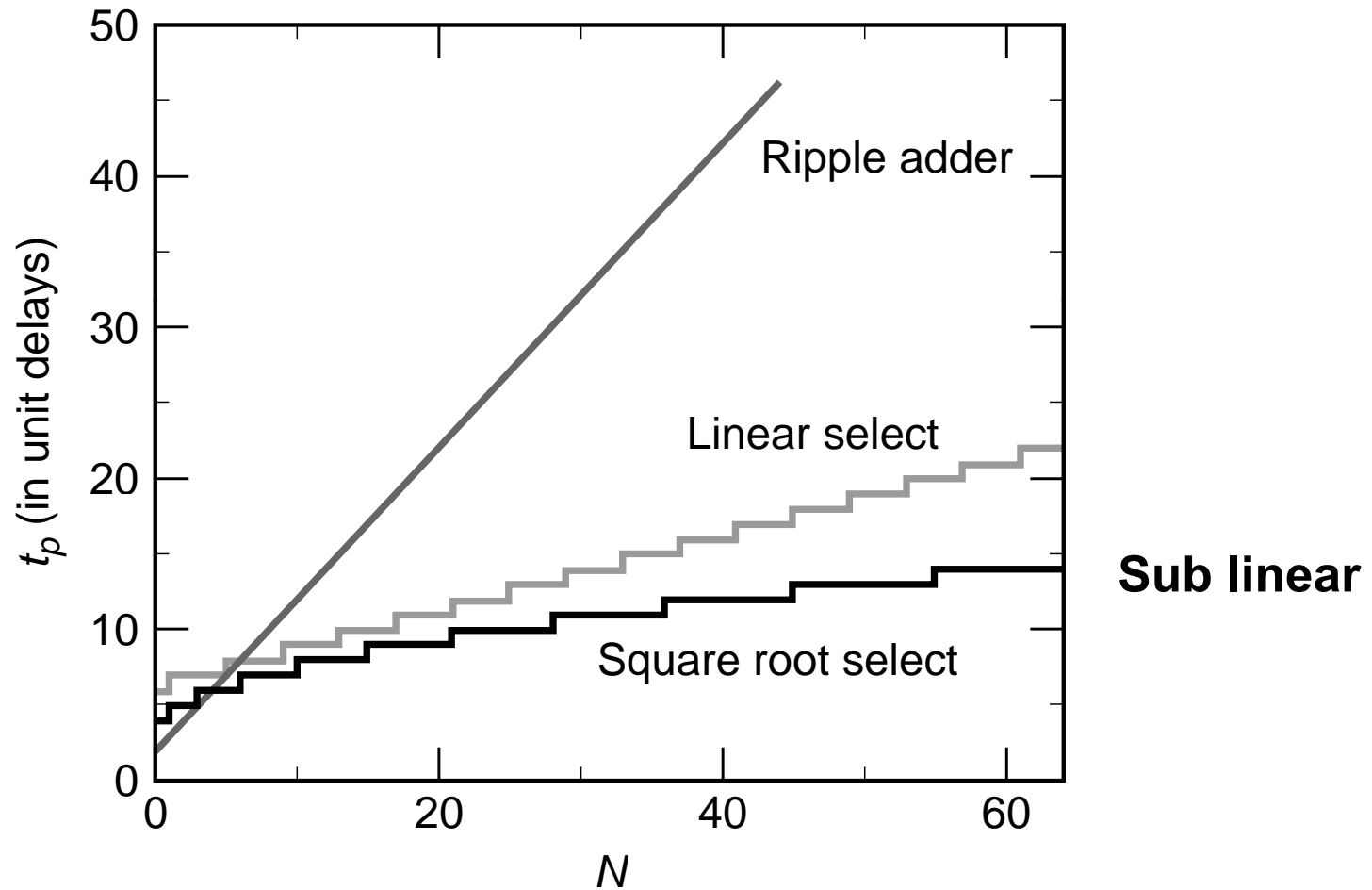

Multiplier Design

- **Multipliers are fundamental building blocks too**
 - **Digital Signal Processing (DSP):** MP3 en/decoder, GSM, GPS, ...
 - **Data processing**
 - **Address arithmetic**
 - ...
- **Good performance is key, often they are the performance bottleneck**
- **Multipliers are complex arrays of adders**
- **Many architectures**
 - **Basic Array Multiplier**
 - **Bit-serial**
 - **Booth-encoding multiplier**
 - **Baugh-Wooley multiplier**
 - **Wallace tree multiplier**
 - ...
- **Design trade-offs, optimization**
 - **Architecture level, Logic level, Circuit level, Layout level**

The Binary Multiplication

$$X = \sum_{i=0}^{M-1} X_i 2^i \quad Y = \sum_{j=0}^{N-1} Y_j 2^j$$

$$Z = X \times Y = \sum_{k=0}^{M+N-1} Z_k 2^k$$

$$= \left(\sum_{i=0}^{M-1} X_i 2^i \right) \left(\sum_{j=0}^{N-1} Y_j 2^j \right)$$


$$= \sum_{i=0}^{M-1} \left(\sum_{j=0}^{N-1} X_i Y_j 2^{i+j} \right)$$

ADD

AND

SHIFT

Example: 42 x 11 = 462

 


Each partial product formed by bitwise AND operation

Partial products are shifted before being added

■ **Conclusion:** similar to decimal multiplication


■
$$X_{10} \times Y_{10} = \sum_{i=0}^{M-1} \left(\sum_{j=0}^{N-1} X_i Y_j 10^{i+j} \right)$$

The Array Multiplier

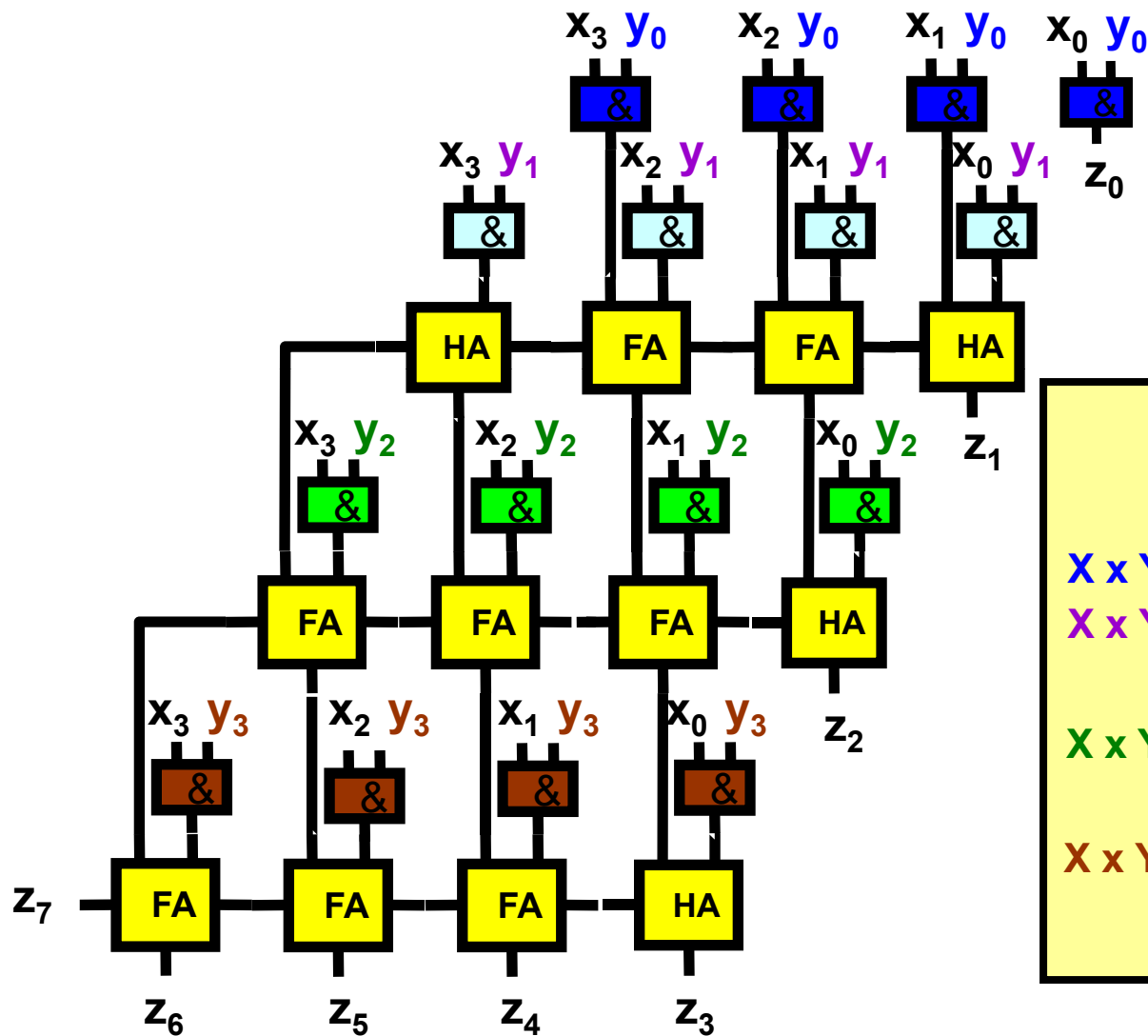

X	1 0 1 0	
Y	1 0 1 1	
	<hr style="width: 100%;"/>	
$X \times Y_0 \times 2^0$	1 0 1 0	x
$X \times Y_1 \times 2^1$	1 0 1 0	
	<hr style="width: 100%;"/>	+
	0 1 1 1 0	
$X \times Y_2 \times 2^2$	0 0 0 0	
	<hr style="width: 100%;"/>	+
	1 0 1 1 1 0	
$X \times Y_3 \times 2^3$	1 0 1 0	
	<hr style="width: 100%;"/>	+
$X \times Y$	1 0 0 1 1 1 0	

The MxN Array Multiplier — Critical Path

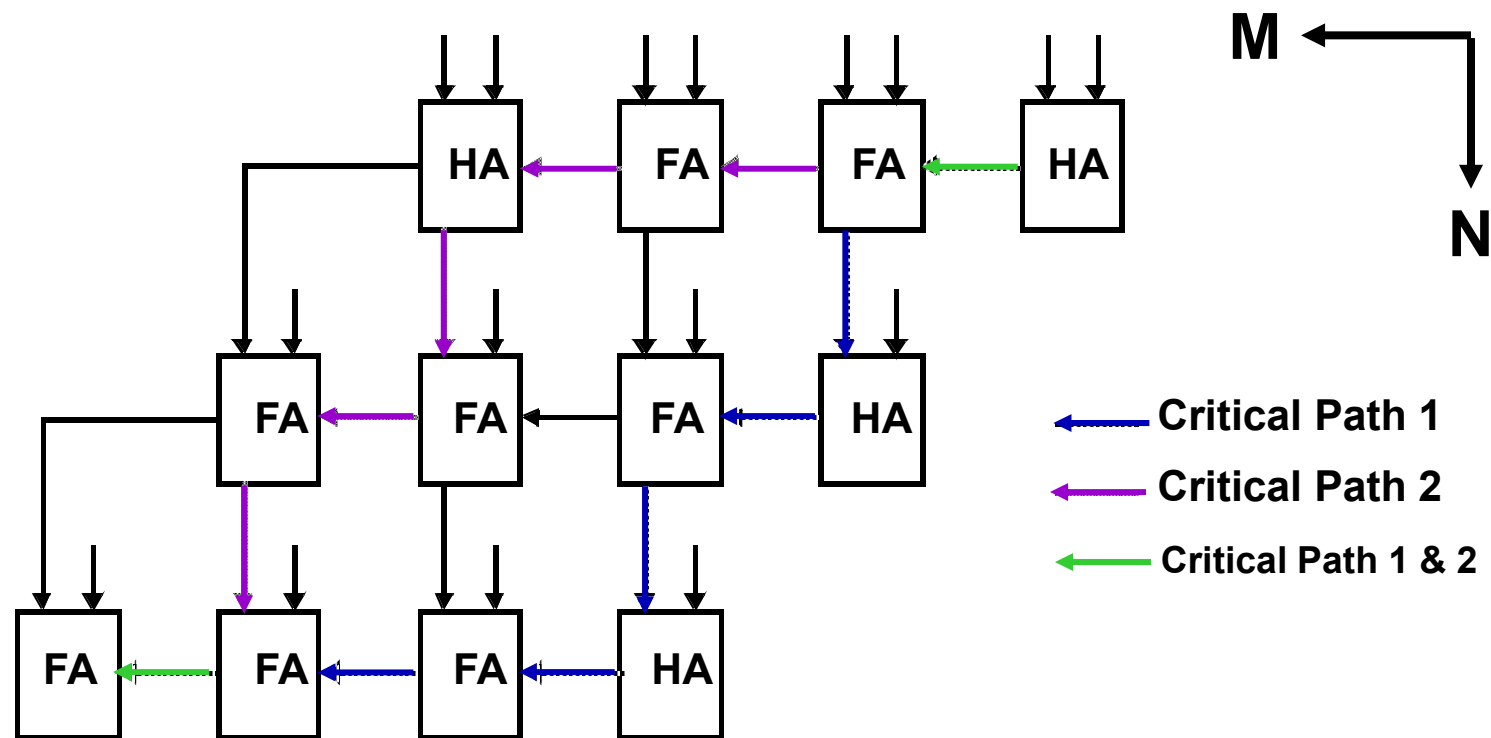


■ $t_{\text{mult}} \approx [(M - 1) + (N - 2)]t_{\text{carry}} + (N - 1)t_{\text{sum}} + t_{\text{and}}$

Requires comparable carry and sum delays

→ Different adder architectures


Layout Strategies (regularity)

Bit-Sliced Design

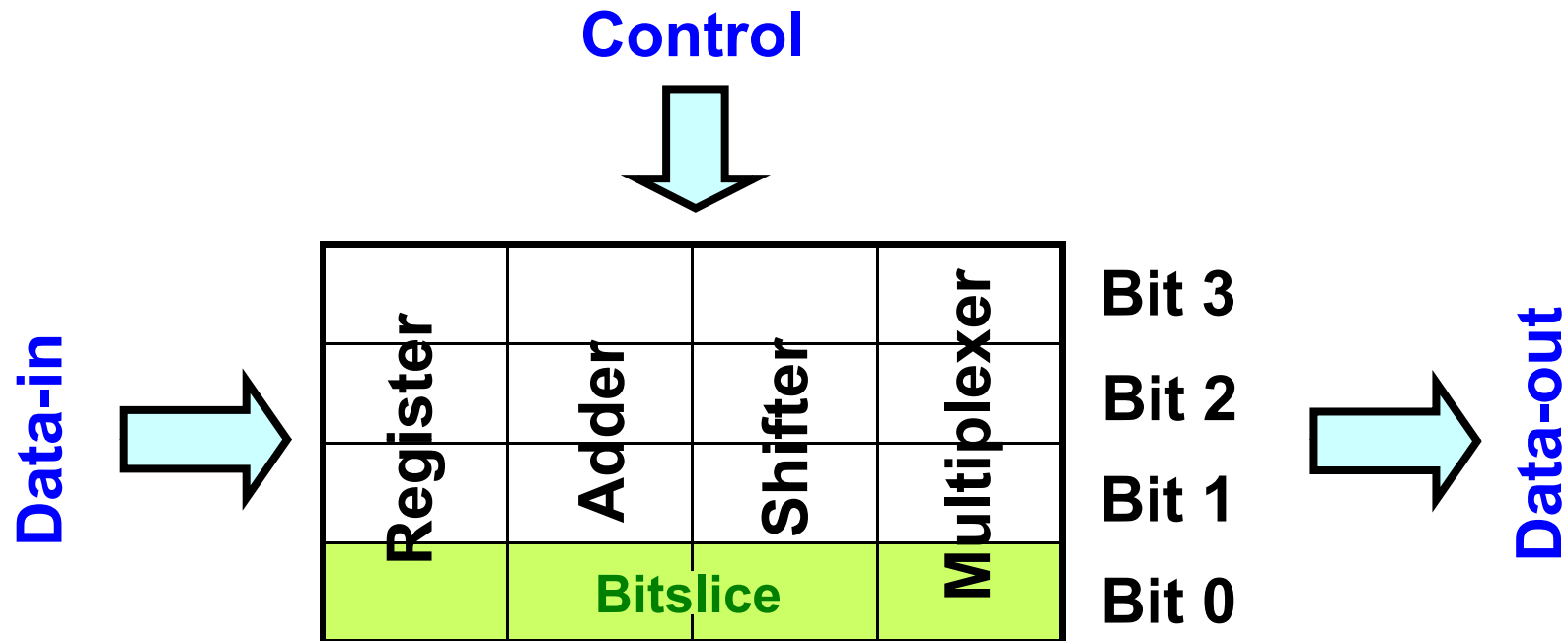


- **Tile** identical processing elements
- Rows for each **bit**
- Columns for each **function**
- **Control** from top (often with *control-slice*)
- (Example orientation)

Layout Strategies for Bit-Sliced Datapaths

 

Approach I —


Signal and power lines parallel

 


Approach II —

Signal and power lines perpendicular


Layout of Bit-sliced Datapaths

 


Layout of Bit-sliced Datapaths (2)

 



Layout of Bit-sliced Datapaths (3)

 

Unoptimized
Area: 4.2mm²

 



With feedthroughs
Area: 3.2mm²

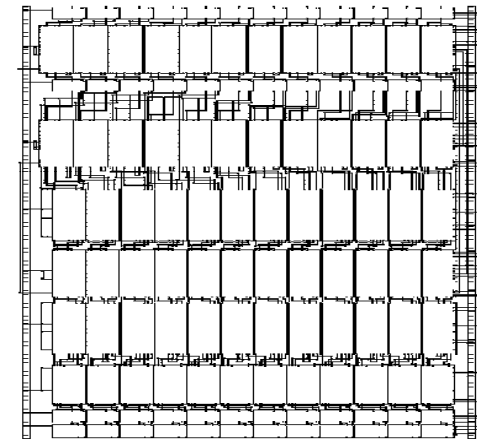 

+ Equalized cell height
Area: 2.2mm²

- **Good layout really counts!**
- **Feedthroughs less (but still) useful with multiple metal layers**

Design as a Trade-Off

  

VLSI Design.

- Select **right structure**
- Determine and optimize **critical timing path** for speed
- Optimize rest for **area** (cost) and/or **power** and/or **design time**
- Consider **layout** aspects

Regularity and **modularity** are a VLSI designer's best friends

Summary.

- **Background on Modular Design**
 - **Hierarchy, reuse, regularity**
 - **Architecture, bit-slicing**
- **Adder Design**
- **Multiplier Design**
- **Shifter Design**
- **Layout Strategies (regularity)**
- **Design as a Trade-Off**

**Got further appreciation of some
system level design issues?**